
EE 207

**Foundation of Electrical and
Computer Engineering**

**By: Eng. Amjad Bou Matar
College Of Engineering
ESE Department
Alfaisal University**

@: aboumatar@alfaisal.edu – Tel: 011 215 7756

Chapter One

Basic Concepts

- This course basically deals with the analysis of electric circuits.
- The most basic quantity used in the analysis of electrical circuits is the electric charge (electron).

Basic Quantities

(1) Electron :electron is a mobile charge carrier.

- The electron is measured in coulomb [C]
- $e = 1.6 \times 10^{-19} \text{ C}$
- Multiple of electrons constitute charge (q).

- The movement of charge (q) over time causes current.

(2) Current :


the time rate of change of charge produces an electrical current

$$i(t) = \frac{dq(t)}{dt} \quad \text{Or} \quad q(t) = \int_{\tau = -\infty}^t i(\tau) d\tau$$

- the electric current is measured in Amper [A]


$$1 \text{ A} = 1 \text{ C} / 1 \text{ sec}$$

- .current convention.

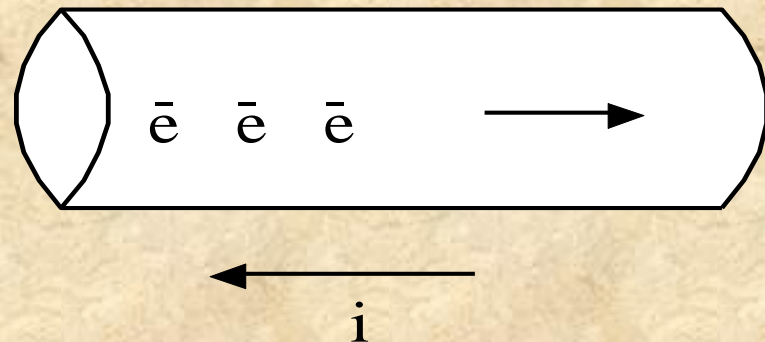


There are 2 types of currents

1. Direct current (DC)

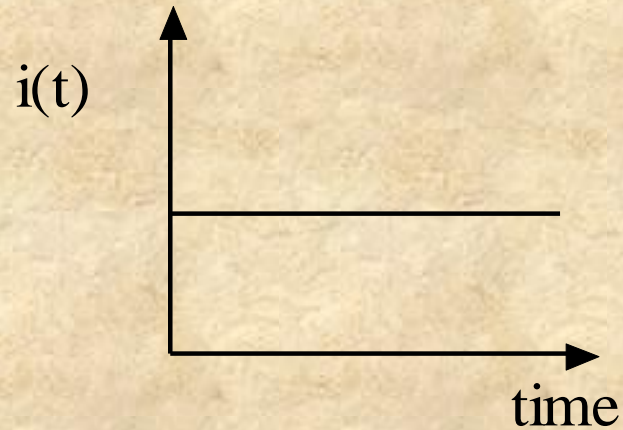

2. Alternating current (AC)

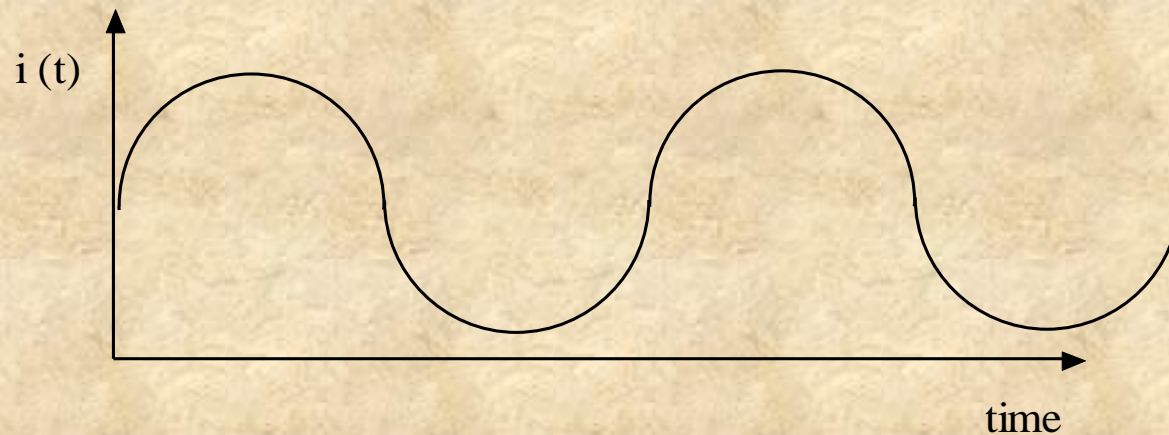

(3) Voltage :

The voltage is defined as the work or energy (in Joules) required per unit charge to move a test charge through an element

$$V = \frac{W}{q}$$

And

$$1V = \frac{1J}{1C}$$

- Since we are dealing with a changing charge and energy, we have

$$v = \frac{dw}{dq}$$

(4) Power :

Power is the time rate of change of energy.

$$P(t) = \frac{dw(t)}{dt}$$

$$P(t) = \frac{dw(t)}{dt} = \frac{dw(t)}{dq} \cdot \frac{dq}{dt}$$

$$P(t) = V(t) i(t)$$

• The unit of power is Watt [W].


• **1 W = 1 V * 1A**

(5) **Energy**: energy can be expressed as

$$w(t) = \int_{t=t_1}^{t_2} p(t) dt = \int_{t=t_1}^{t_2} v(t) i(t) dt$$

Passive sign convention

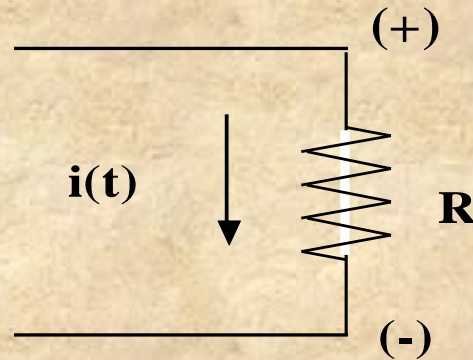
Current flow from the positive to the negative terminal.



- Power can be absorbed or supplied by an element.
- Power is absorbed (or dissipated) by an element if the sign of power is $(+)$
- Power is supplied (delivered or generated) by an element if the sign of power is $(-)$

Circuit Active Elements:

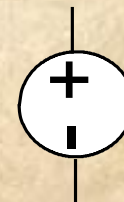There are 4 types of active elements (sources):




1. Independent voltage source:

It is a 2-terminal sources that maintains a specific voltage across its terminals regardless of the current through it

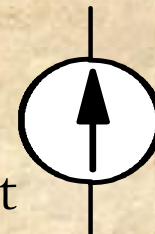2. Independent current source:

It is a 2-terminal sources that maintains a specific current through it regardless of the voltage across it terminals.



3. Dependent voltage source:

It is a 2-terminal sources that generates a voltage that is determined by a voltage or current at a specified location in the circuit.




4. Dependent current source:

It is a 2-terminal sources that generates a current that is determined by voltage or current at a specified location in the circuit.



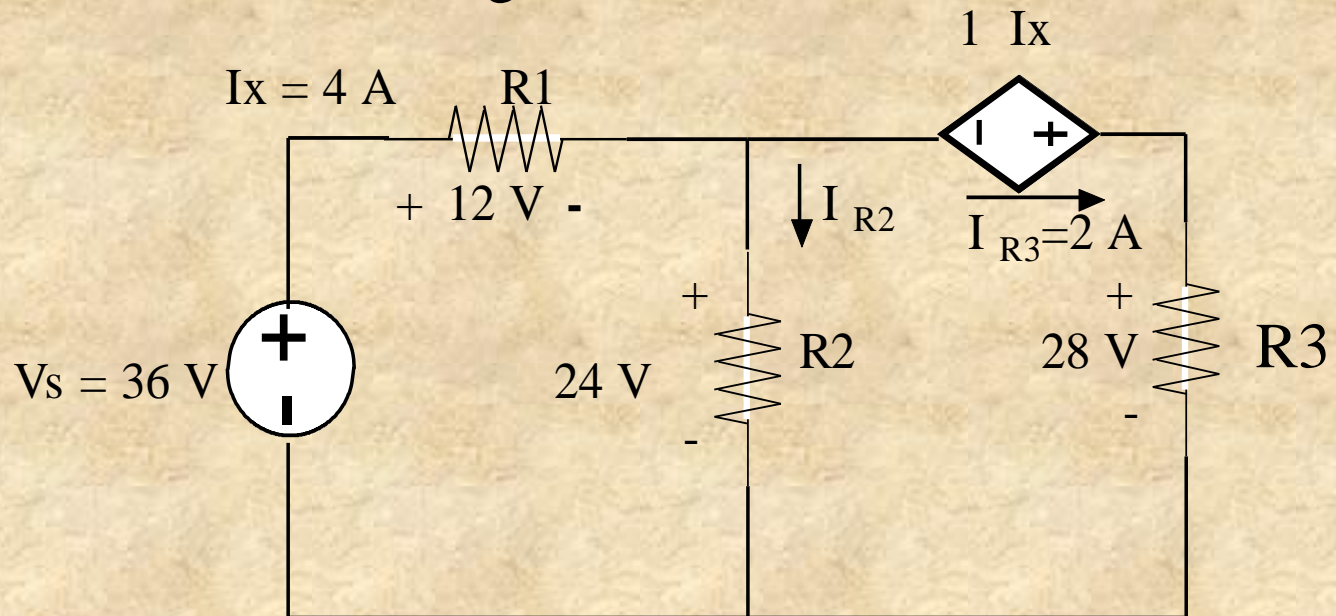Example :

Compute the power that is absorbed or supplied by each of the elements in the following circuit



$$P_{v_s} = V_s I_x = (36)(-4) = -144\text{W} \text{ (supplies)}$$

$$P_{R1} = V_{R1} I_x = (12)(4) = 48\text{W} \text{ (absorbs)}$$

$$P_{R2} = V_{R2} I_{R2} = V_{R2} (I_x - I_{R3}) = \\ (24)(4 - 2) = 48\text{W} \text{ (absorbs)}$$

$$P_{D_s} = V_{D_s} I_{R3} = (1I_x)(I_{R3}) = (4)(-2) = -8\text{W} \text{ (supplies)}$$

$$P_{R3} = V_{R3} I_{R3} = (28)(2) = 56\text{ W} \text{ (absorbs)}$$

Important Units

<u>QUANTITY</u>	<u>SYMBOL</u>	<u>UNIT</u>	<u>ABBREV.</u>
Length	l	meter	m
Current	I, i	ampere	A
Temperature	T	kelvin	K
Mass	m	kilogram	kg
Time	t	second	s

Important Units

Voltage	$V, v,$	volt	V
Charge	Q, q	coulomb	C
Resistance	R	ohm	Ω
Power	P, p	watt	W
Capacitance	C	farad	F
Inductance	L	henry	H
Frequency	f	hertz	Hz
Magnetic Flux	Φ	weber	Wb
Mag. Flux Density	B	tesla	T

Unit Conversions

<u>UNIT</u>	<u>MULTIPLY BY</u>	<u>TO GET</u>
in	0.0254	m
ft	0.3048	m
mi	1.609	km
lb	4.448	N
hp	746	W
kWh	3.6×10^6	J
ft-lb	1.356	J

Prefixes For Engineering Notation

POWER OF 10

PREFIX

SYMBOL

10^{12}

tera

T

10^9

giga

G

10^6

mega

M

10^3

kilo

k

10^{-3}

milli

m

10^{-6}

micro

μ

10^{-9}

nano

n

10^{-12}

pico

p