

---

**EE 207**

**Foundation of Electrical and  
Computer Engineering**

**By: Eng. Amjad Bou Matar  
College Of Engineering  
ESE Department  
Alfaisal University**

**@: [aboumatar@alfaisal.edu](mailto:aboumatar@alfaisal.edu) – Tel: 011 215 7756**

# Chapter 2

## Resistive Circuits


### Ohm's law :

The voltage across a resistor is directly proportional to the current flowing through it.

$$V(t) = R i(t) \quad R \geq 0$$

The symbol of ohm is ( $\Omega$ )

$$1\Omega = \frac{1V}{1A}$$

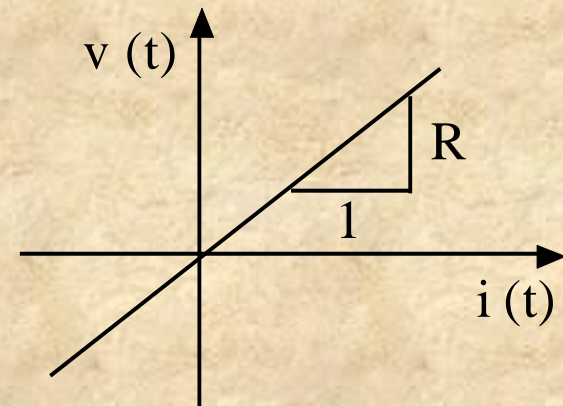

The instantaneous power  $P(t)$ :

$$P(t) = v(t)i(t) = R i(t)i(t)$$

$$= R i^2(t) = v(t) \frac{v(t)}{R} = \frac{v^2(t)}{R}$$

$$\therefore P(t) = v(t)i(t) = R i^2(t) = \frac{v^2(t)}{R}$$

**Note:** Last equation says that the power at a resistor is always positive

⇒ Resistors always absorb power.

The inverse of resistance is conductance

$$G = \frac{1}{R}$$

The unit of conductance is Siemens (S)

$$1\text{S} = \frac{1\text{A}}{1\text{V}}$$

The current can be also expressed as

$$i(t) = G V(t)$$

And the instantaneous power is


$$P(t) = v(t)i(t) = \frac{i(t)}{G} i(t) = \frac{i^2(t)}{G}$$

$$P(t) = v(t)i(t) = v(t)G v(t) = G v^2(t)$$

$$\Rightarrow v(t)i(t) = \frac{i^2(t)}{G} = G v^2(t)$$

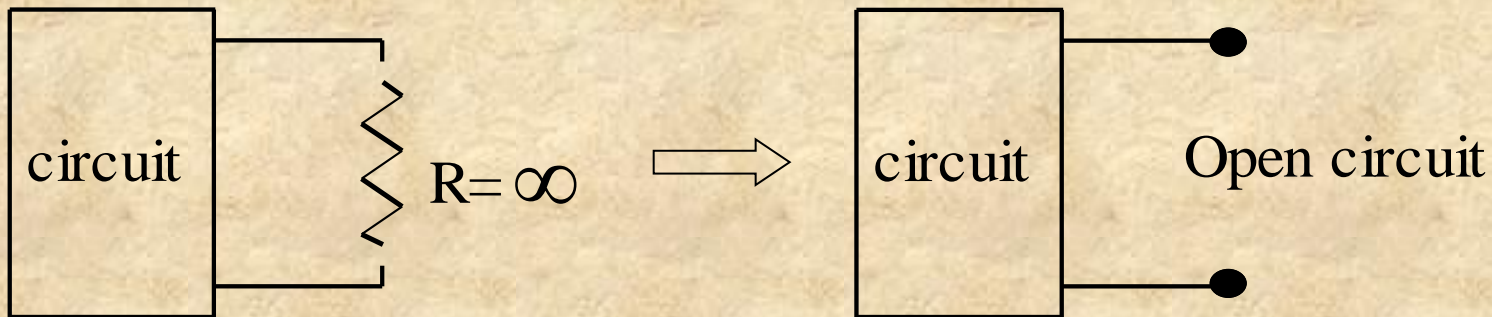
## Open and short Circuits

Open circuit (  $R = \infty$  )  $\implies G = 0$



$$i(t) = \frac{v(t)}{R} = \frac{v(t)}{\infty} = 0$$

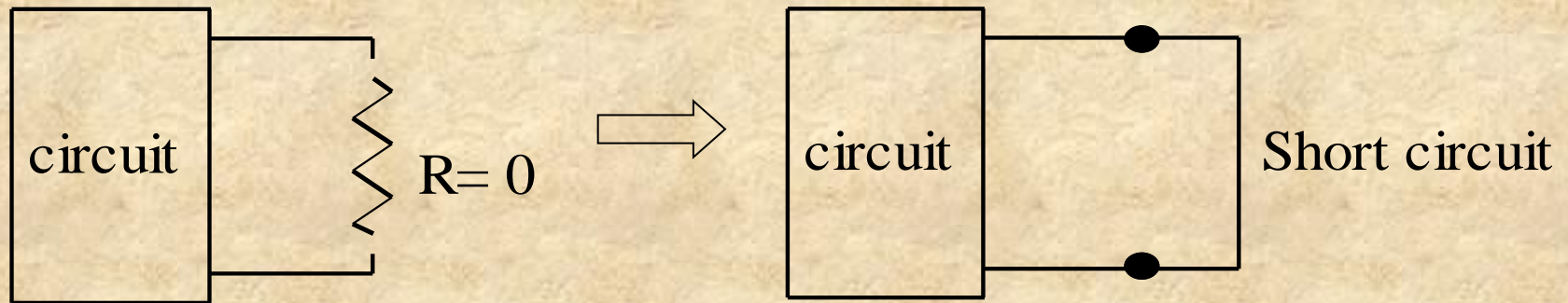
Short circuit ( $R = 0$ )  $\Rightarrow$   $G = \infty$



$$v(t) = Ri(t) = 0 * i(t) = 0$$

Example :

Consider the circuit:

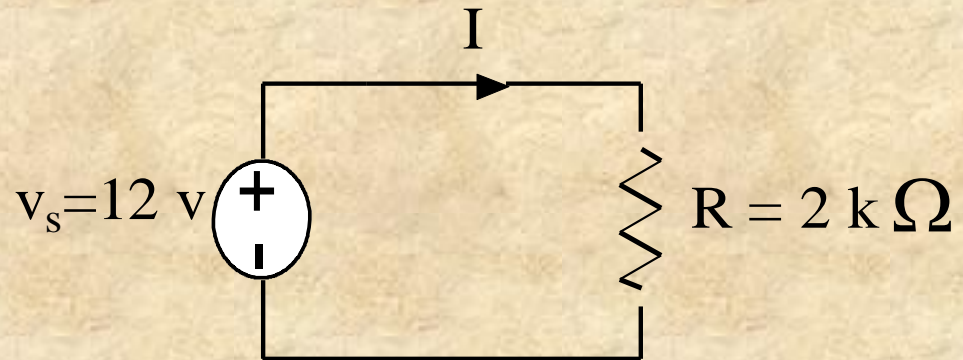

Find the current and power absorbed by the resistor

$$I = \frac{v_s}{R} = \frac{12 \text{ v}}{2 \text{ k}\Omega} = 6 \text{ mA}$$

$$P = v_R I = (12)(6 \text{ mA}) = 72 \text{ mW}$$

## Example:

The power absorbed by a  $10\text{ k}\Omega$  resistor in the circuit is  $3.6\text{ mW}$ .

Find voltage and current in the resistor.

$$P = V_s I = I^2 R$$


$$I^2 = \frac{P}{R}$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{(3.6 * 10^{-3}) / (10 * 10^3)}$$

$$I = \sqrt{3.6 * 10^{-7}} = 0.6\text{ mA}$$

$$V = IR = (0.6\text{ mA})(10\text{ k}\Omega)$$


$$V = 6\text{ V}$$

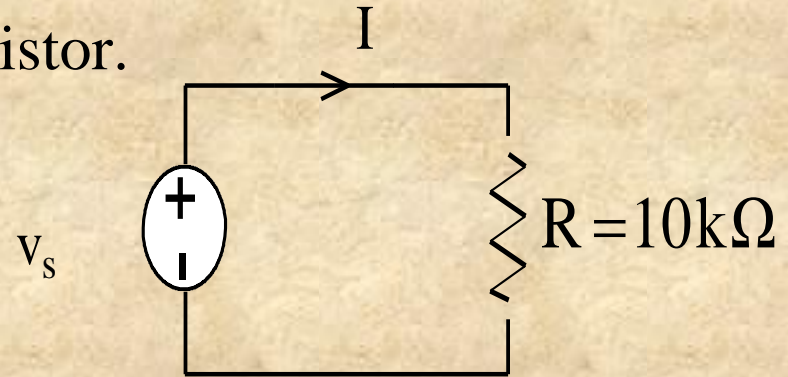


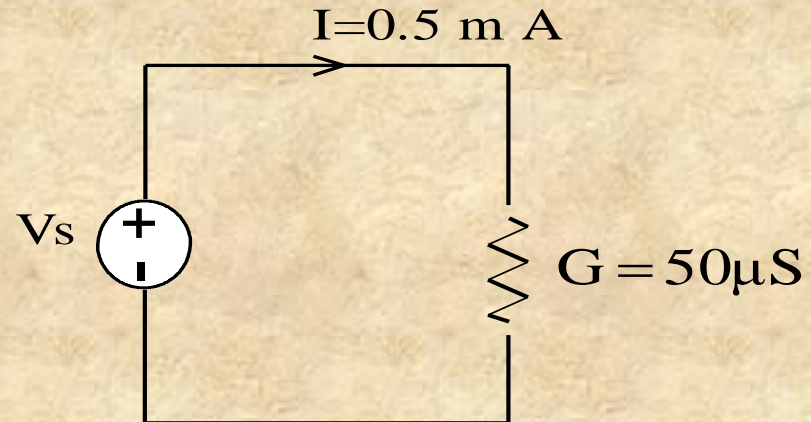
## Example :

Find the value of the voltage source and the power absorbed by the resistance



$$G = 50\mu\text{S} \implies R = 1/G = 2 \times 10^4$$

$$V_s = IR = (0.5 \text{ mA})(20 \times 10^4 \Omega) = 10 \text{ V}$$

$$P_R = IV = (10 \text{ V})(0.5 \text{ mA}) = 5 \text{ m W}$$

## Example :

Find R and the voltage across  
The resistor?


$$P = V I_s$$

$$V = \frac{P}{I_s} = \frac{80 * 10^{-3} \text{ W}}{4 * 10^{-3} \text{ A}}$$

$$V = 20\text{V}.$$

$$V = IR = (4 * 10^{-3} \text{ A})R$$
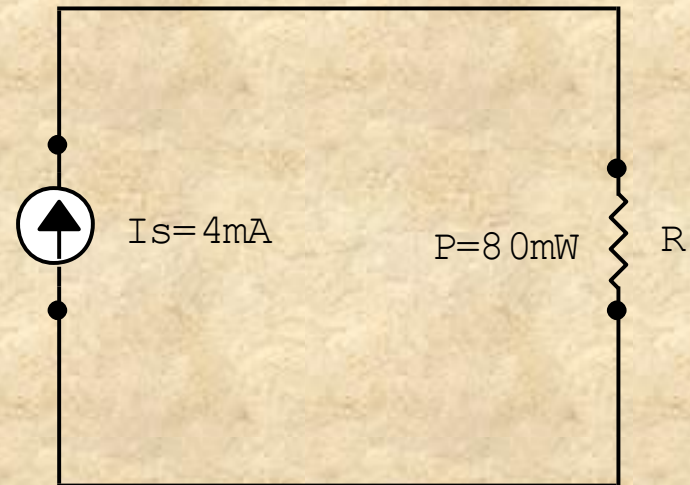
$$R = \frac{V}{I} = \frac{20 \text{ V.}}{4 * 10^{-3} \text{ A}} = 5\text{k}\Omega$$



# Kirchoff's Laws:

## (1) kirchoff's current law (KCL) :

the sum of all currents entering any node is zero.

$$\Rightarrow \sum_{k=1}^N i_k(t) = 0$$

Where N= number of currents.

## Example:

Write the KCL equation


Here we have (4) nodes:

$$\text{At node (1) : } i_1(t) + i_2(t) = i_5(t)$$

$$\text{At node (2) : } i_2(t) + 50i_2(t) = i_3(t)$$

$$\text{At node (3) : } 50i_2(t) + i_4(t) = i_1(t)$$
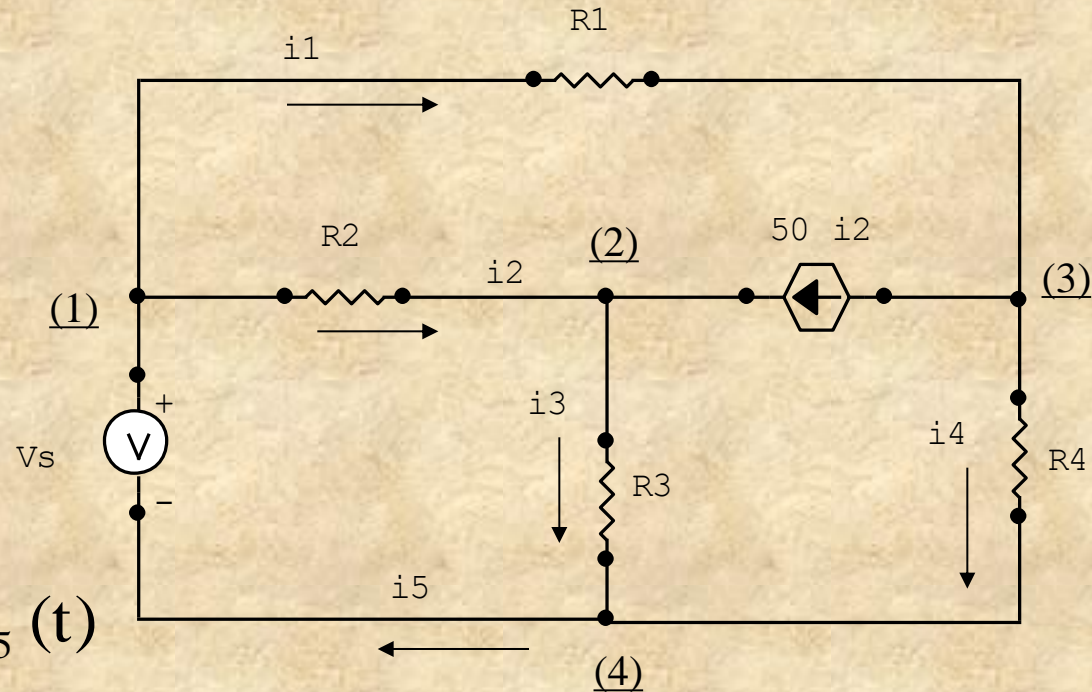
$$\text{At node (4) : } i_3(t) + i_4(t) = i_5(t)$$




## (2) Kirchoff's voltage Law (KVL):

The sum of the voltage around any loop is zero.

$$\sum_{k=1}^N v_k(t) = 0 \quad \Rightarrow \quad N = \# \text{ of voltage}$$

### Example:

Find  $V_{R3}$  ? using KVL

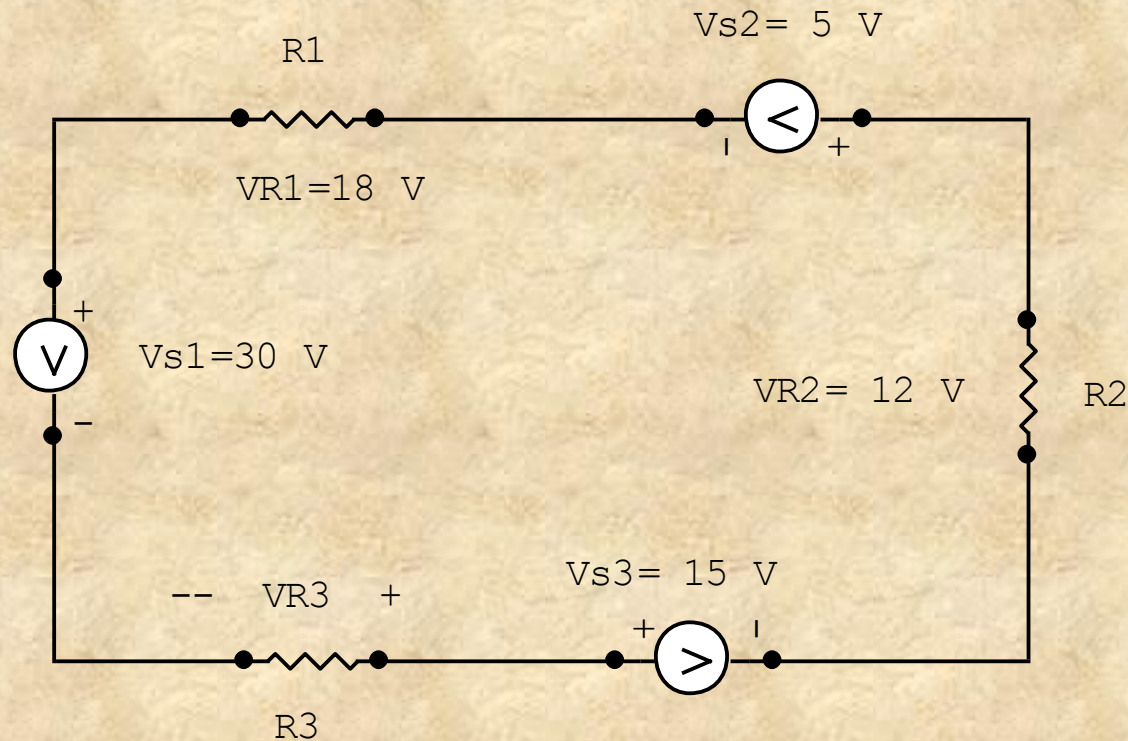

$$-30 + 18 - 5 + 12 - 15 + V_{R3} = 0$$

$$V_{R3} = 20 \text{ V}$$

## Example :


Find the KVL equation for the two paths abda and bcdb

Path abda:

$$V_{R1} + V_{R2} - V_s = 0$$

Path bcdb:

$$20 V_{R1} + V_{R3} - V_{R2} = 0$$

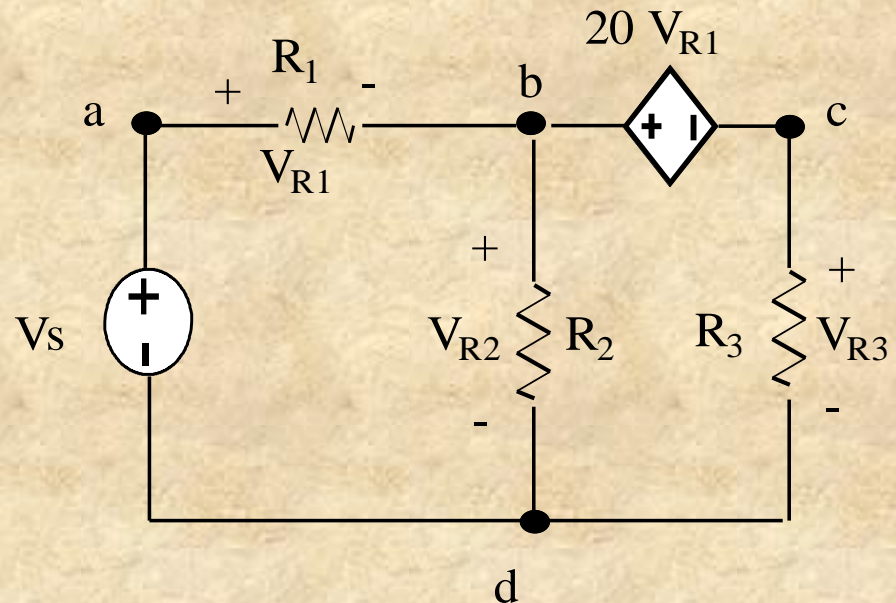

# Single Loop circuits


We will discuss (2) issues :

## 1. Voltage divider rule:

Voltage is divided between resistor in direct proportion to their resistance

$$v_1(t) = \frac{R_1}{R_1 + R_2} v(t)$$

$$v_2(t) = \frac{R_2}{R_1 + R_2} v(t)$$

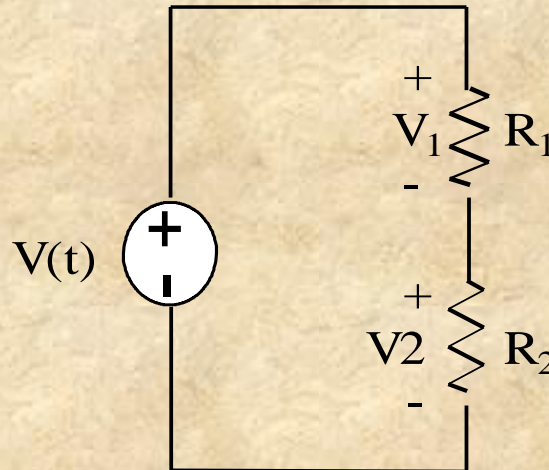


How?

$$v_1 = R_1 i = R_1 \left( \frac{v}{R_1 + R_2} \right)$$

$$v_1 = \frac{R_1}{R_1 + R_2} v$$
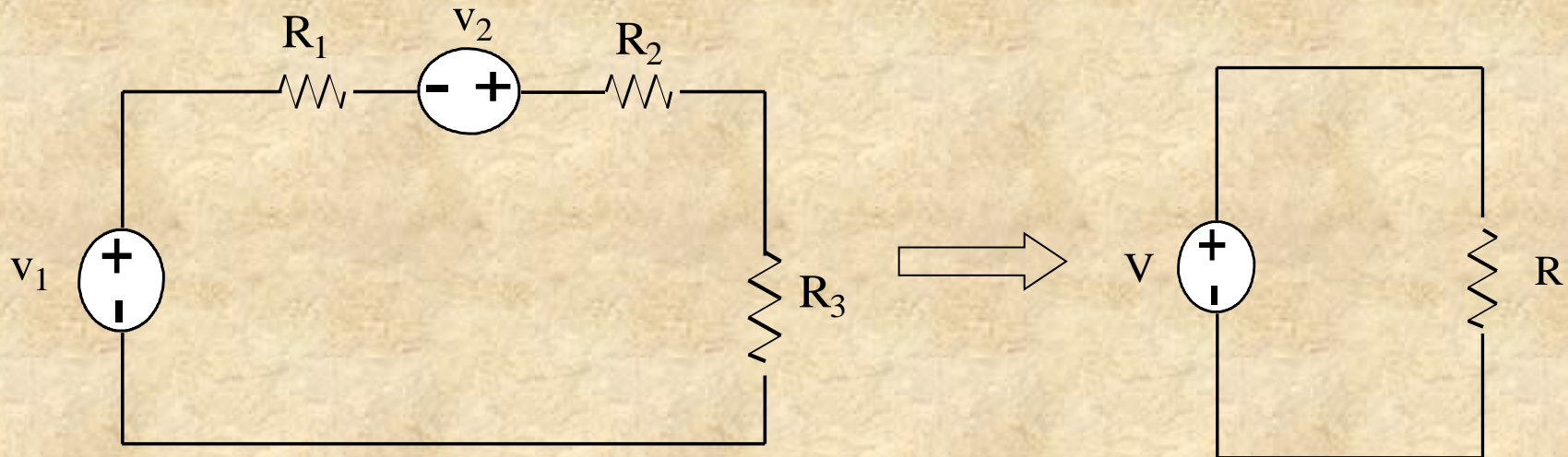
## Multi Sources / resistors :

- Source can be added  $v=v_1+v_2+\dots$
- Resistors can be added  $R= R_1+R_2+\dots$



Where:

$$v = v_1 + v_2$$

$$R = R_1 + R_2 + R_3$$




# Single Node-Pair circuits :

We will discuss (2) issues:

## 1. Current-divider Rule .

$$i_1(t) = \frac{R_2}{R_1 + R_2} i(t)$$

$$i_2(t) = \frac{R_1}{R_1 + R_2} i(t)$$

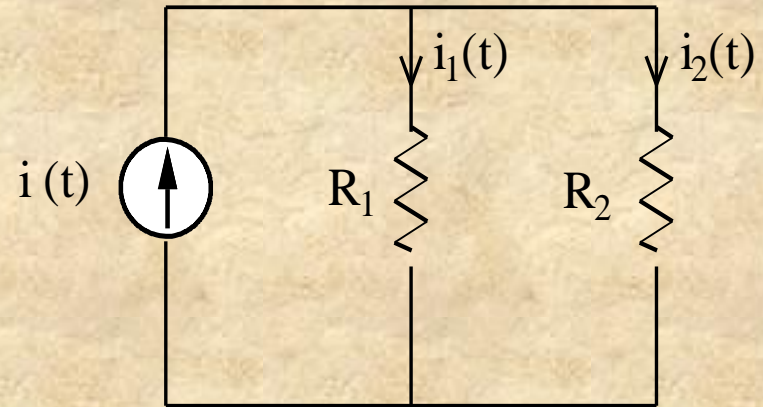

**Why ??**

$$v = i_1 R_1 = i_2 R_2$$

$$\therefore i_1 = \frac{R_2}{R_1} i_2$$

$$i = i_1 + i_2 \Rightarrow i_2 = i - i_1$$

$$i_1 = \frac{R_2}{R_1} (i - i_1)$$


$$i_1 \left(1 + \frac{R_2}{R_1}\right) = \frac{R_2}{R_1} i$$

$$i_1 \left(\frac{R_1 + R_2}{R_1}\right) = \frac{R_2}{R_1} i$$

$$i_1 = \frac{R_2}{R_1 + R_2} i$$

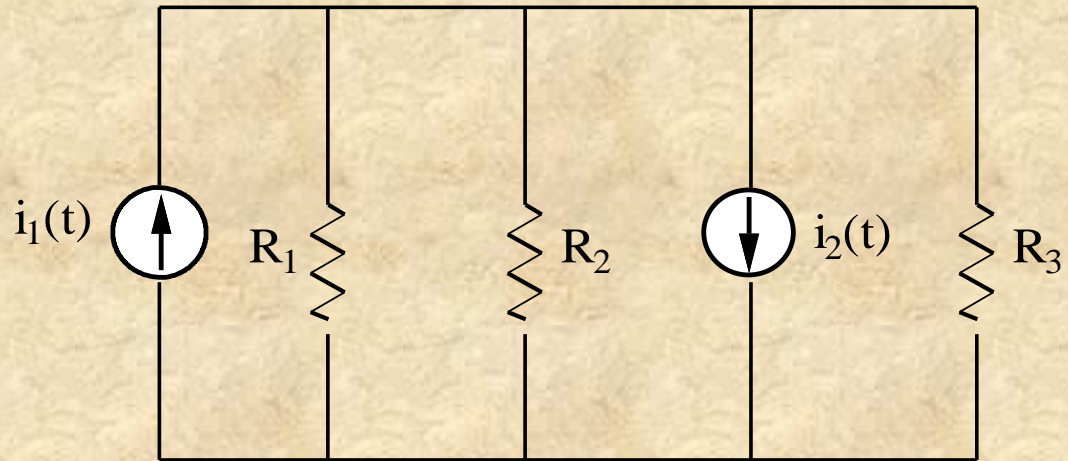
## **2. Multiple sources/resistors :**

- Current source can be added.
- Resistors can be added as reciprocals



$$i(t) = i_1(t) + i_2(t)$$
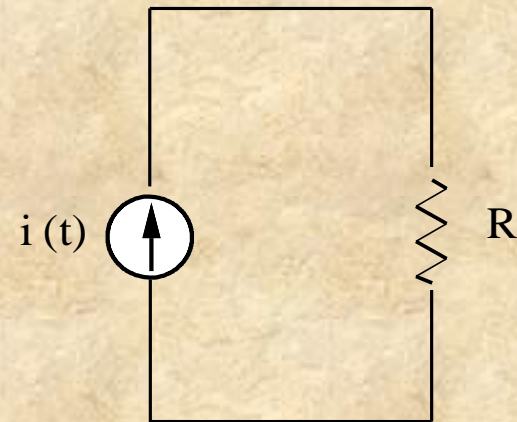
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



## Series and parallel resistors :


Series :  $R = R_1 + R_2 + \dots + R_N \quad \Rightarrow R_s = \sum_{k=1}^N R_k$

Parallel


$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$
$$\frac{1}{R_p} = \sum_{k=1}^N \frac{1}{R_k}$$

## Example :


Find equivalent resistance

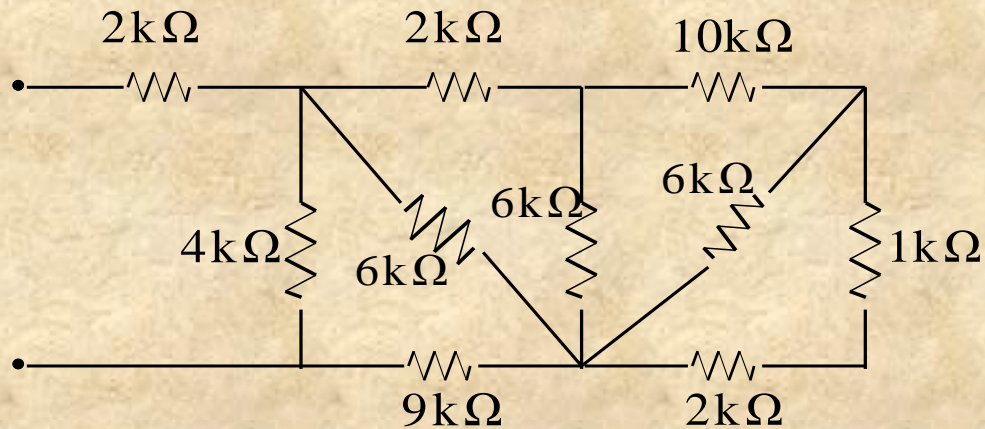

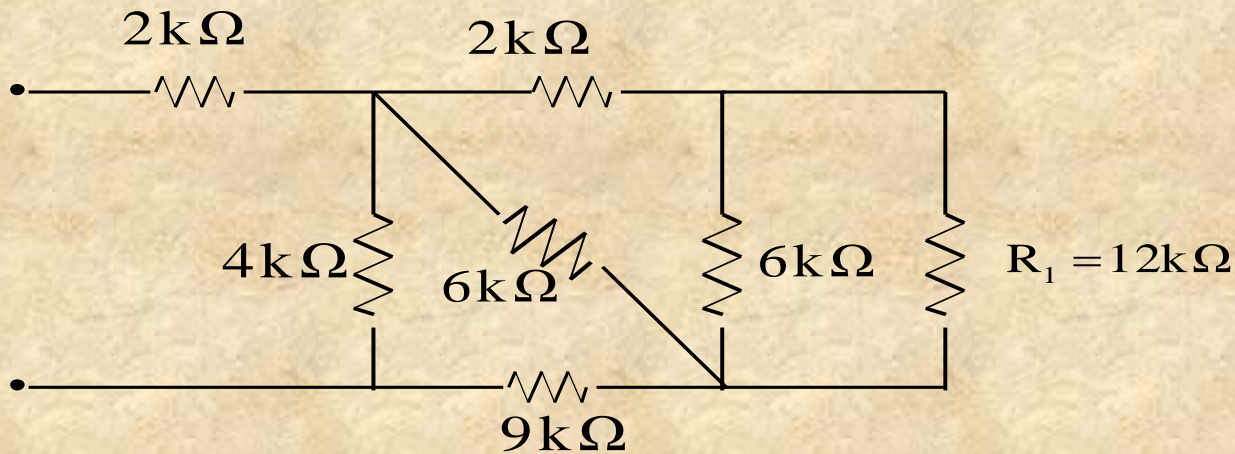
$$R_1 = \{ [(1\text{k}\Omega) + (2\text{k}\Omega)] \parallel 6\text{k}\Omega \} + 10\text{k}\Omega$$



$$R_2 = [12k // 6k] + 2k = 6k$$

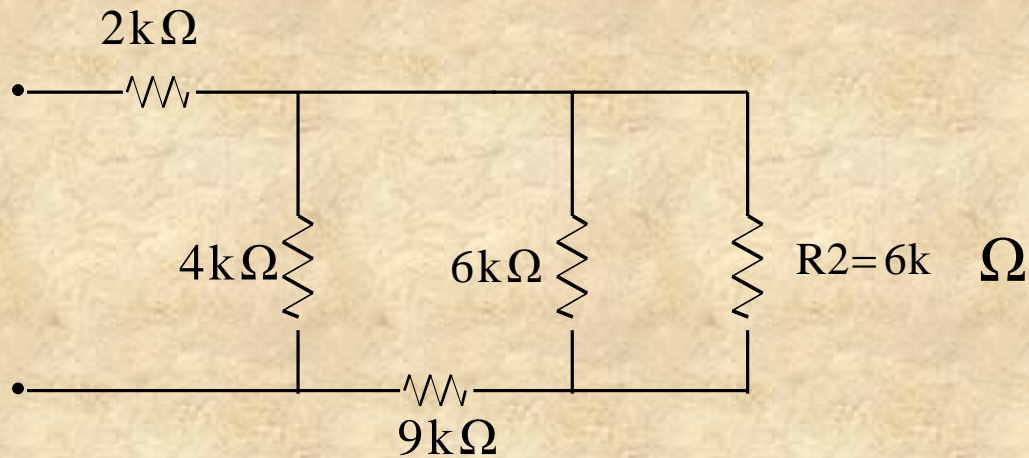

$$R_3 = (6k // 6k) = 3k\ \Omega$$

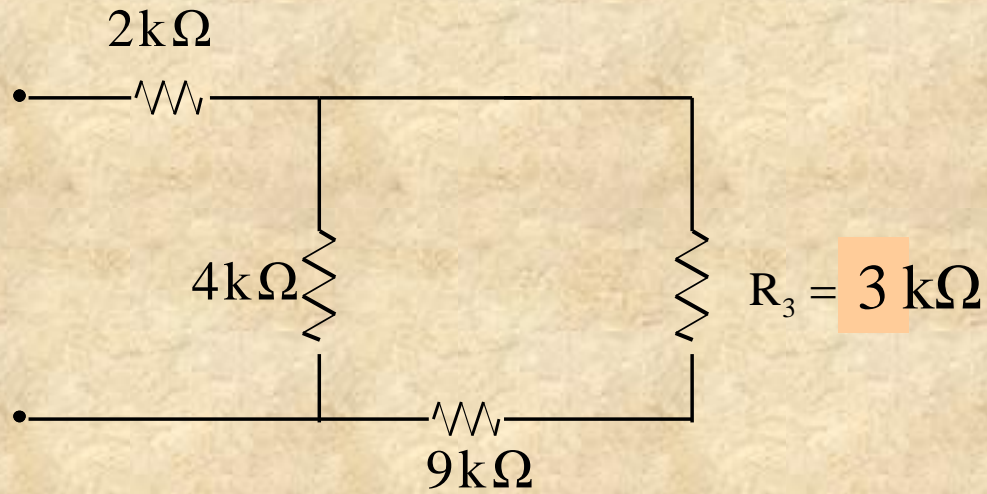


$$R_{\text{eq}} = (12\text{k} \parallel 4\text{k}) + 2\text{k} = 5\text{k}$$




## Example :

Find all currents and voltages

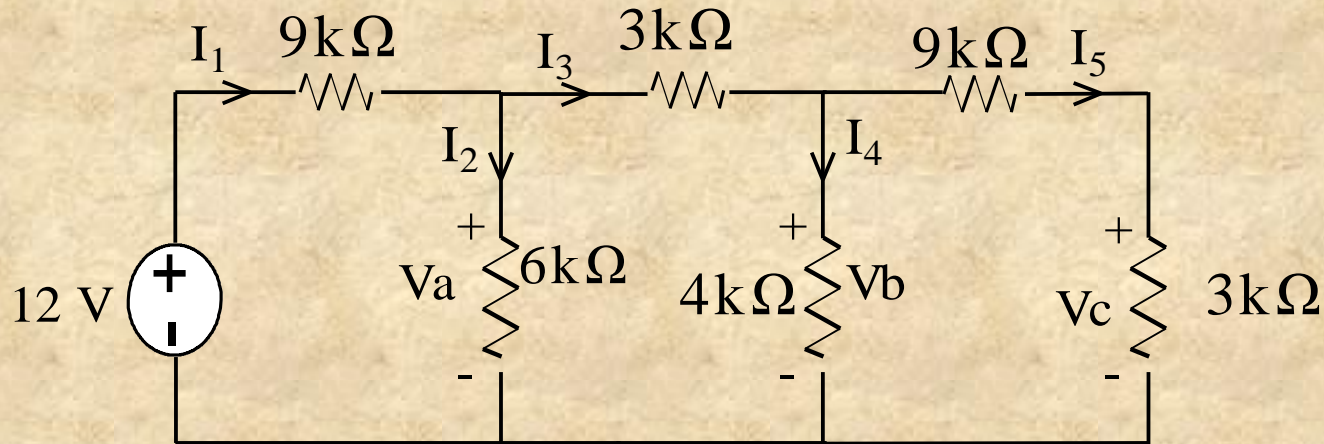

The equivalent circuit is :

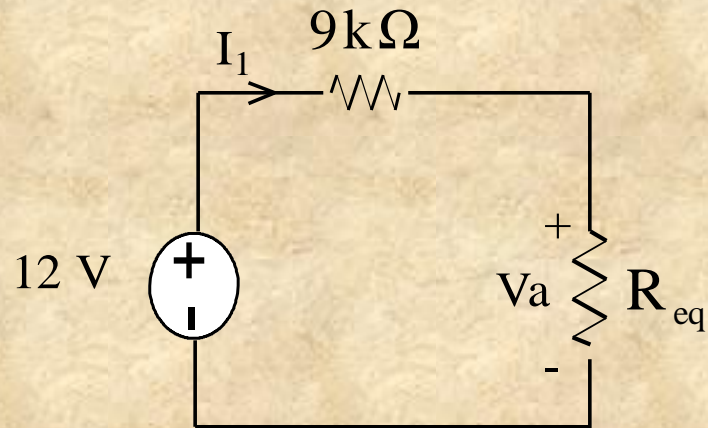



$$\begin{aligned} R_{eq} &= \left[ \left[ (3k + 9k) // 4k \right] + 3k \right] // 6k \\ &= 3k\Omega \end{aligned}$$

$$I_1 = \frac{12V}{9k + 3k} = 1mA \quad \Rightarrow V_a = R_{eq} I_i = 3V$$

$$\therefore I_2 = \frac{V_a}{6k\Omega} = \frac{3}{6k} = \frac{1}{2}mA$$

$$I_3 = I_1 - I_2 \quad \Rightarrow I_3 = 1mA - \frac{1}{2}mA = \frac{1}{2}mA$$

$$V_{3k\Omega} = I_3 (3k\Omega) = \left(\frac{1}{2} \text{ mA}\right) (3k\Omega) = 1.5 \text{ V}$$

$$\therefore V_b - V_a + V_{3k\Omega} = 0$$

$$V_b - 3 + 1.5 = 0 \quad \Rightarrow V_b = 1.5 \text{ V}$$

$$I_5 = \frac{V_b}{9k + 3k} = \frac{1.5}{12k} = \frac{1}{8} \text{ mA}$$

$$V_c = I_5 (3k\Omega) = \frac{1}{8} \text{ mA} (3k\Omega) = \frac{3}{8} \text{ V}$$


## Example :

Find the source voltage  $V_o$  if  $I_4 = 1/2 \text{ m A}$  ?

$$V_b = I_4 (6k) = \left(\frac{1}{2} \text{ m A}\right) (6k \Omega) = 3 \text{ V}$$

$$\therefore I_3 = \frac{V_b}{3k} = \frac{3}{3k} = 1 \text{ m A}$$
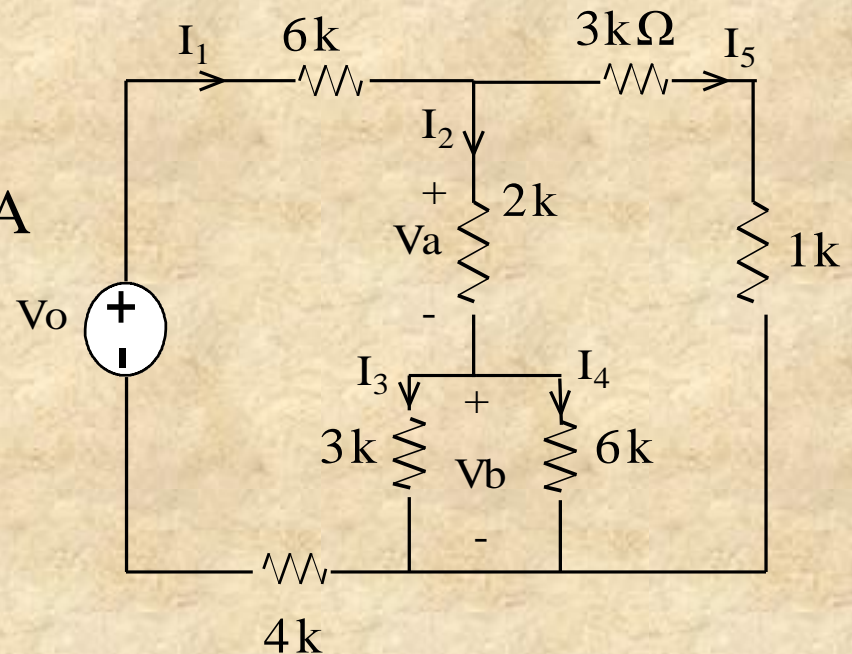
$$I_2 = I_3 + I_4 = 1 \text{ m A} + \frac{1}{2} \text{ m A} = 1.5 \text{ m A}$$



$$\therefore V_a = 2\text{k}\Omega I_2 = (2\text{k})(1.5\text{m}) = 3\text{V}$$

$$I_5 = \frac{V_a + V_b}{3\text{k} + 1\text{k}} = \frac{3 + 3}{4\text{k}} = 1.5\text{mA}$$


$$\therefore I_1 = I_2 + I_5 = 1.5\text{mA} + 1.5\text{mA} = 3\text{mA}$$

$$V_0 = (6\text{k}\Omega)I_1 + V_a + V_b + (3\text{k}\Omega + 1\text{k}\Omega)I_1$$

$$V_0 = 6\text{k}(3\text{m}) + 3 + 3 + 4\text{k}(3\text{m})$$


$$V_0 = 18 + 6 + 12 = 36$$

$$V_0 = 36\text{V}$$

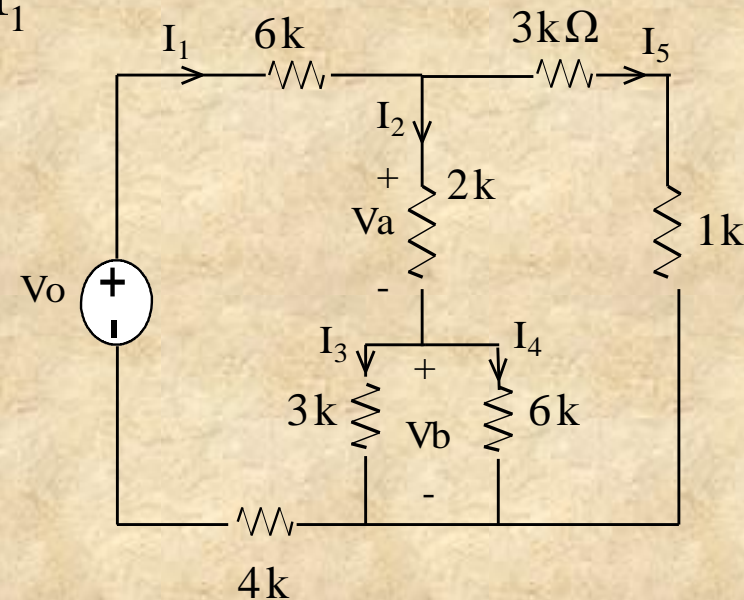

## Example :

Find  $V_0$  ? Using KVL

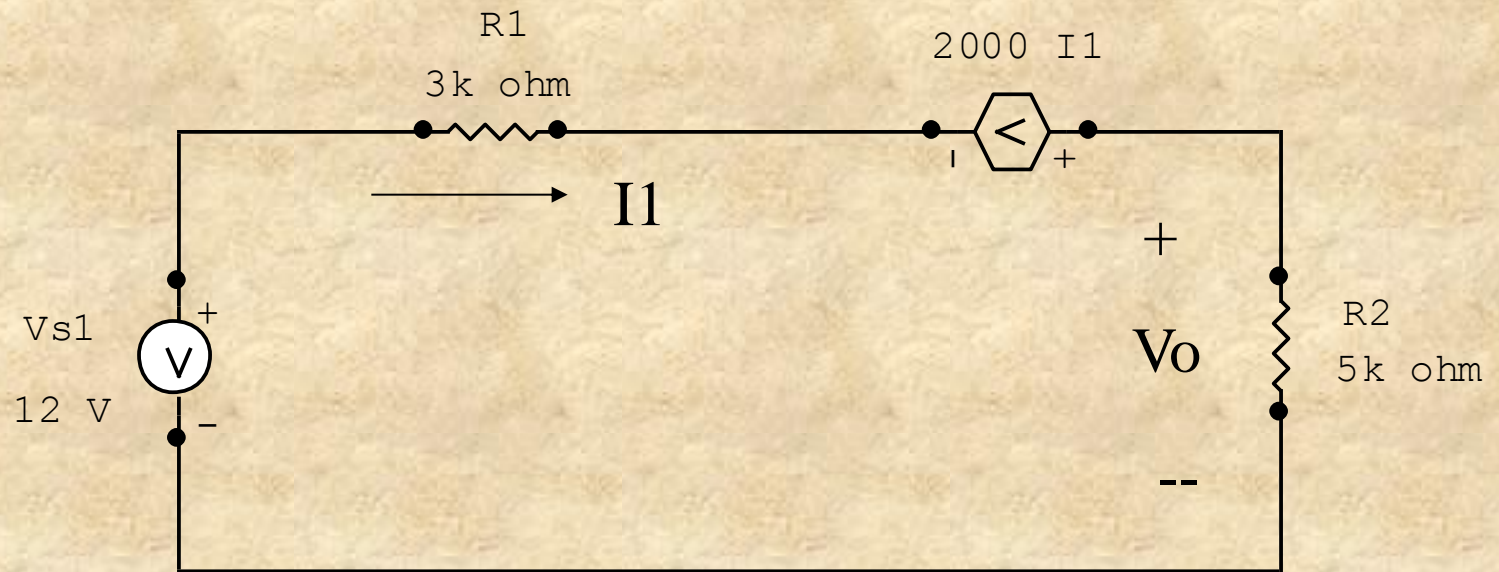

$$-12 + 3\text{ k } (I_1) - 2000 I_1 + 5\text{ k } (I_1) = 0$$


$$6\text{ k } I_1 = 12 \quad \Rightarrow I_1 = 2\text{ m A}$$

$$V_0 = (5\text{ k } \Omega) (I_1) = (5\text{ k }) (2\text{ m})$$

$$V_0 = 10\text{ V}$$

## Example:

Find  $V_0$  using KCL:

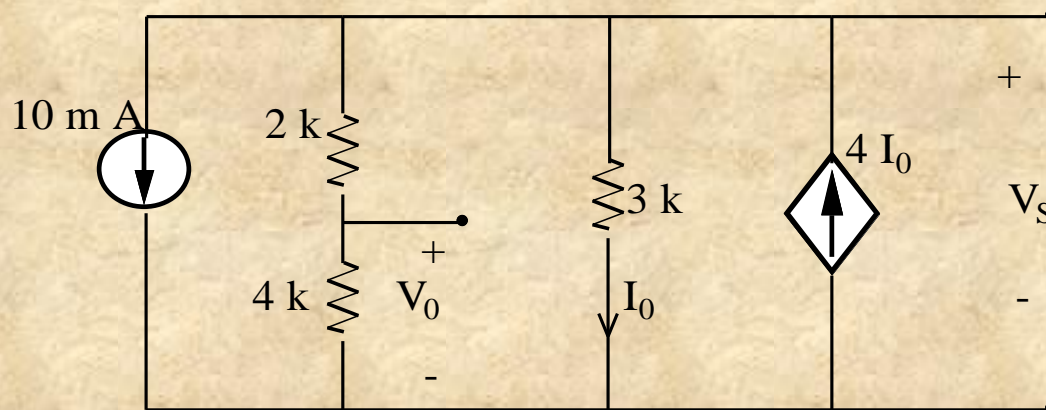

$$10 \text{ m} + \frac{V_s}{6 \text{ k}} + \frac{V_s}{3 \text{ k}} - 4 \left( \frac{V_s}{3 \text{ k}} \right) = 0$$


$$V_s \left[ \frac{1}{6 \text{ k}} + \frac{1}{3 \text{ k}} - \frac{4}{3 \text{ k}} \right] = -10 \text{ m A}$$

$$V_s = 12 \text{ V}$$

$$V_0 = \frac{4 \text{ k}}{2 \text{ k} + 4 \text{ k}} V_s = \frac{2}{3} (12) = 8 \text{ V}$$

## Example:

Find  $V_0$  using KVL

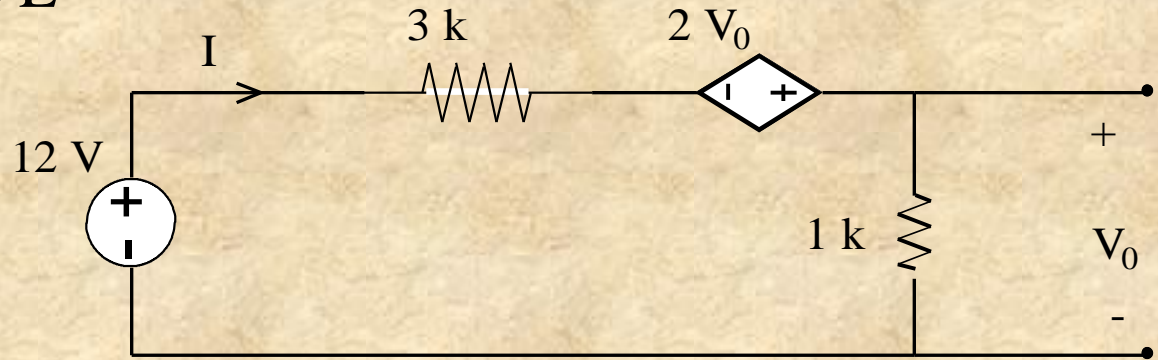

$$-12 + (3\text{k})I - 2V_0 + V_0 = 0$$

$$-V_0 + (3\text{k})I - 12 = 0$$

$$I = \frac{V_0}{1\text{k}}$$


$$-V_0 + (3\text{k})\left(\frac{V_0}{1\text{k}}\right) = 12$$

$$-V_0 + 3V_0 = 12$$

$$V_0 = 6\text{ V}$$

## Example:

Find  $V_0$  in the network

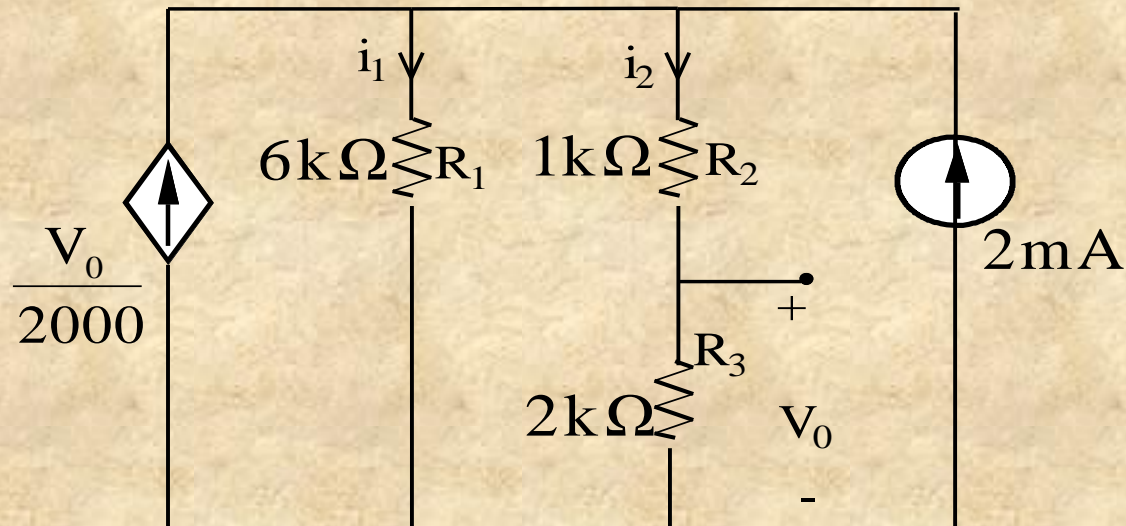

$$\frac{V_0}{2000} - i_1 - i_2 + 2\text{ mA} = 0$$

$$R_1 i_1 = (R_2 + R_3) i_2$$

$$\text{Also } (6\text{ k}\Omega) i_1 = (3\text{ k}\Omega) i_2$$

$$\therefore i_1 = \frac{1}{2} i_2$$



$$\therefore \frac{V_0}{2000} - \frac{1}{2}i_2 - i_2 + 2 \text{ mA} = 0$$

$$\frac{V_0}{2000} - \frac{3}{2}i_2 + 2 \text{ mA} = 0$$

$$\therefore V_0 = R_3 i_2 \Rightarrow i_2 = \frac{V_0}{2k}$$

$$\therefore \frac{V_0}{2k} - \frac{3}{2} \left( \frac{V_0}{2k} \right) + 2 \text{ mA} = 0$$

$$\frac{1}{2} \left( \frac{V_0}{2k} \right) = 2 \text{ mA} \Rightarrow V_0 = 8 \text{ V}$$