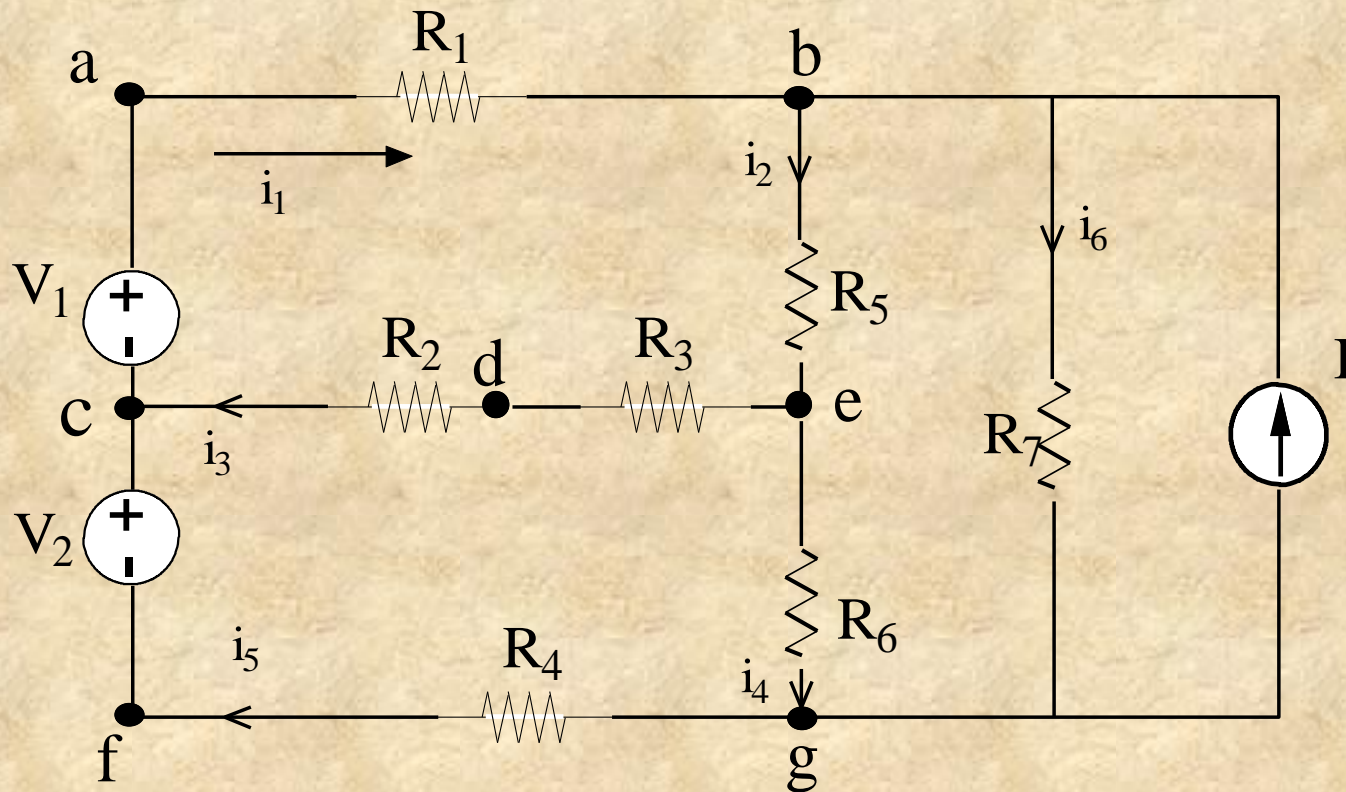


Chapter (3)

Nodal and loop analysis

Consider the following circuit:



Definitions:

Node :

A point where two or more circuit elements join

Ex. a,b,c,d,e,f,g

Essential Node:

A node where three or more circuit element join

Ex. b,c,e,g

Path:

A trace of adjoining elements with no elements included more than once

1. $V_1-R_1-R_5-R_6$
2. $R_5-R_6-R_4-V_2$,etc

Branch:

A path that connects any two nodes.

Ex. R_1 , V_1 , R_1 - R_5 , etc

Essential Branch:

A path that connects two essential nodes without passing through an essential node.

Ex. V_1 - R_1 , R_5 , R_2 - R_3 , V_2 - R_4 , ...

Loop :

A path whose last node is the same as its starting node

Ex. (1) V_1 - R_1 - R_5 - R_3 - R_2

(2) V_1 - R_1 - R_5 - R_6 - R_4 - V_2

Mesh :

A loop that doesn't enclose any other loops.

Ex. V_1 - R_1 - R_5 - R_3 - R_2

Ex. V_2 - R_2 - R_3 - R_6 - R_4 , ...


- In chapter (2) we studied circuits containing a single loop or a single node-pair
 - Such circuits can be solved easily by one algebraic equation.
 - Here , we will study circuit containing multiple node and multiple loops
 - Hence we will introduce (2) analysis techniques :
1. **Nodal analysis**
 2. **Loop analysis**

(1) Nodal Analysis :

Nodal analysis : is a technique in which KCL is used to determine the nodes' voltages at all essential nodes with respect to the reference node.

• Here , node voltage is defined as the voltage of a given node with respect to a reference node

Example:

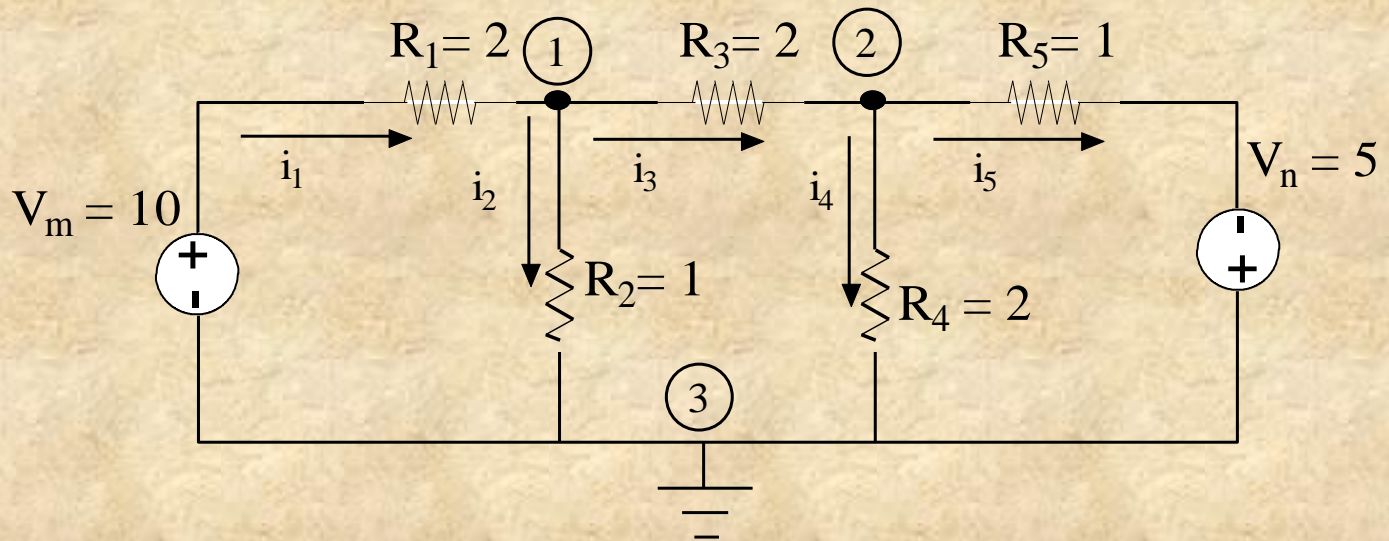

Essential nodes : 1,2,3

Consider (3) to be the reference node (ground)

At (1) apply KCL:

$$i_1 - i_2 - i_3 = 0$$

$$\frac{V_m - V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} = 0$$

$$\frac{10 - V_1}{2} - \frac{V_1}{1} - \frac{V_1 - V_2}{2} = 0$$

$$5 - \frac{V_1}{2} - V_1 - \frac{V_1}{2} + \frac{V_2}{2} = 0$$

$$5 - 2V_1 + \frac{V_2}{2} = 0$$

$$4V_1 - V_2 = 10 \dots\dots (1)$$

At (2), Apply KCL:

$$i_3 - i_4 - i_5 = 0$$

$$\frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} - \frac{V_2 - V_n}{R_5} = 0$$

$$\frac{(V_1 - V_2)}{2} - \frac{V_2}{2} - \frac{(V_2 + 5)}{1} = 0$$

$$\frac{V_1}{2} - 2V_2 - 5 = 0$$

$$V_1 - 4V_2 = 10 \dots\dots (2)$$

$$\begin{bmatrix} 4 & -1 \\ 1 & -4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$

$$A V = B \Rightarrow V = A^{-1} B \Rightarrow V_1 = 2$$

$$V_2 = -2$$

Note :


Number of equations = $N-1$

Where :

N is the number of essential nodes

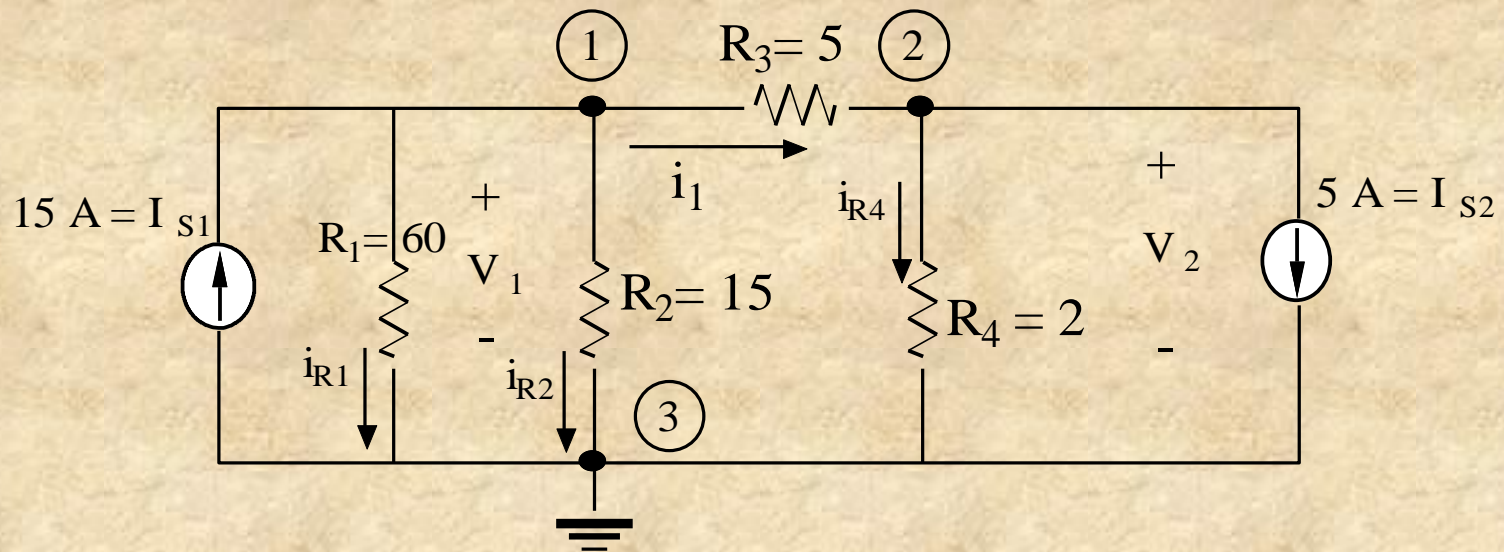Example :

Circuit with only independent current source



Find V_1, V_2 and i

of essential node = $N=3$

Select (3) as ground (reference node)

of KCL equations = $N-1 = 2$

At node (1) apply KCL

$$I_{s1} - i_{R1} - i_{R2} - i_1 = 0$$

$$15 - \frac{V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} = 0$$

$$15 - \frac{V_1}{60} - \frac{V_1}{15} - \frac{V_1}{5} + \frac{V_2}{5} = 0$$

$$\left(\frac{1}{5} + \frac{1}{15} + \frac{1}{60}\right) V_1 - \frac{1}{5} V_2 = 15$$

$$\frac{12 + 4 + 1}{60} V_1 - \frac{1}{5} V_2 = 15$$

$$\frac{17}{60} V_1 - \frac{1}{5} V_2 = 15 \quad \dots\dots(1)$$

At node (2)

$$i_1 - i_{R4} - I_{s2} = 0$$

$$\frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} - 5 = 0$$

$$\frac{V_1 - V_2}{5} - \frac{V_2}{2} - 5 = 0$$

$$2V_1 - 2V_2 - 5V_2 - 50 = 0$$

$$2V_1 - 7V_2 = 50 \quad \dots\dots(2)$$

$$\begin{bmatrix} \frac{17}{60} & -\frac{1}{5} \\ \frac{2}{2} & -\frac{7}{-7} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 15 \\ 50 \end{bmatrix}$$

$$V_1 = 60 \text{ V}$$


$$V_2 = 10 \text{ V}$$

$$i_1 = \frac{V_1 - V_2}{R} = \frac{60 - 10}{5} = 10 \text{ A}$$

Example :

Circuit with dependent current source

Find I_0

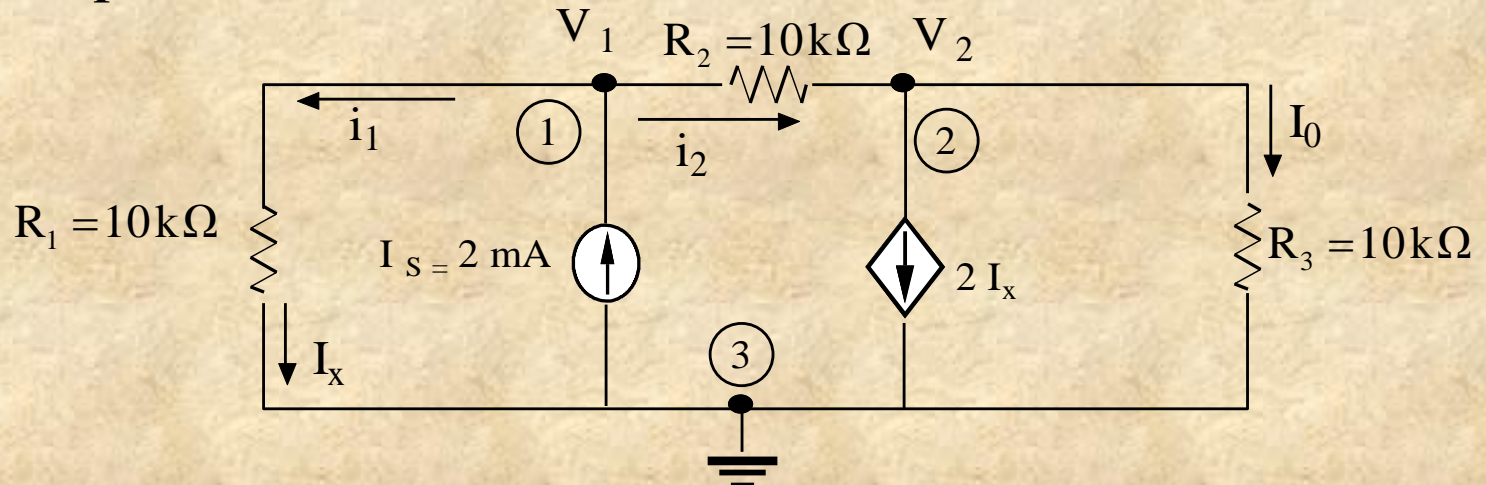

of essential nodes = $N=3$

Choose (3) to be reference node (ground)

We have $N-1 = 2$ KCL equation
at node(1) and(2)

At node (1) , apply KCL

$$I_s - i_1 - i_2 = 0$$

$$2 \text{ m A} - \frac{V_1}{R_1} - \frac{V_1 - V_2}{R_2} = 0$$

$$2 \text{ m A} = \frac{V_1}{10\text{k}} + \frac{V_1 - V_2}{10\text{k}} = \frac{V_1}{5\text{k}} - \frac{V_2}{10\text{k}}$$

$$0.2 V_1 - 0.1 V_2 = 2 \text{ A} \quad \dots\dots(1)$$

At node (2) apply KCL,

$$i_2 - 2I_x - I_0 = 0$$

$$i_2 - 2I_x - I_0 = 0$$

$$\frac{V_1 - V_2}{R_2} - 2I_x - I_0 = 0$$

where $I_x = i_1 = \frac{V_1}{R_1}$

$$I_0 = \frac{V_2}{R_3}$$

$$\Rightarrow \frac{V_1 - V_2}{10k} - 2 \frac{V_1}{10k} - \frac{V_2}{10k} = 0$$

$$1 V_1 + 2 V_2 = 0 \quad \dots\dots(2)$$

$$\begin{bmatrix} 0.2 & -0.1 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

$$V_1 = 8 \text{ V}$$


$$V_2 = -4 \text{ V}$$

$$\Rightarrow I_0 = \frac{V_2}{R_3} = \frac{-4}{10\text{k}} = -0.4 \text{ mA}$$

Example:

(circuit with independent voltage source)

Find i_a, i_b, i_c, i_d, i_e

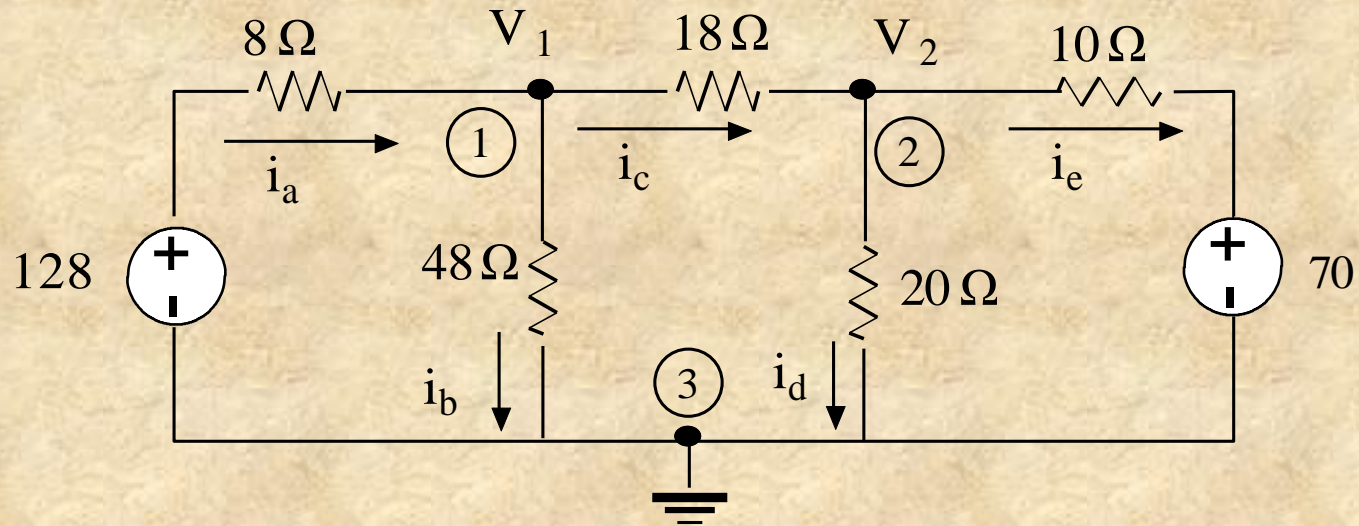

$$N=3 \implies N-1 = 2$$

Choose (3) to be ground

KCL at (1)

$$\frac{128 - V_1}{8} - \frac{V_1}{48} - \frac{V_1 - V_2}{18} = 0$$

$$16 - \frac{V_1}{8} - \frac{V_1}{48} - \frac{V_1}{18} + \frac{V_2}{18} = 0$$

$$0.201388 V_1 - \frac{1}{18} V_2 = 16 \quad \dots\dots(1)$$

KCL at (2)

$$\frac{V_1 - V_2}{18} - \frac{V_2}{20} - \frac{V_2 - 70}{10} = 0$$

$$\frac{1}{18} V_1 - 0.20555 V_2 = -7 \quad \dots\dots(2)$$

$$\begin{bmatrix} 0.201338 & \frac{-1}{18} \\ \frac{1}{18} & -0.2055 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 16 \\ -7 \end{bmatrix}$$

$$V_1 = 96 \text{ V}$$

$$V_2 = 60 \text{ V}$$

$$\therefore i_a = \frac{128 - V_1}{8} = \frac{128 - 96}{8} = 4 \text{ A}$$

$$i_b = \frac{V_1}{48} = \frac{96}{48} = 2 \text{ A}$$

$$i_c = \frac{V_1 - V_2}{18} = \frac{96 - 60}{18} = 2 \text{ A}$$

$$i_d = \frac{V_2}{20} = \frac{60}{20} = 3 \text{ A}$$

$$i_e = \frac{V_2 - 70}{10} = -1 \text{ A}$$

$$\therefore i_a = \frac{128 - V_1}{8} = \frac{128 - 96}{8} = 4 \text{ A}$$

$$i_b = \frac{V_1}{48} = \frac{96}{48} = 2 \text{ A}$$

$$i_c = \frac{V_1 - V_2}{18} = \frac{96 - 60}{18} = 2 \text{ A}$$


$$i_d = \frac{V_2}{20} = \frac{60}{20} = 4 \text{ A}$$

$$i_e = \frac{V_2 - 70}{10} = -1 \text{ A}$$

Special case:

What if a branch between two essential non-reference node contain a voltage source ?

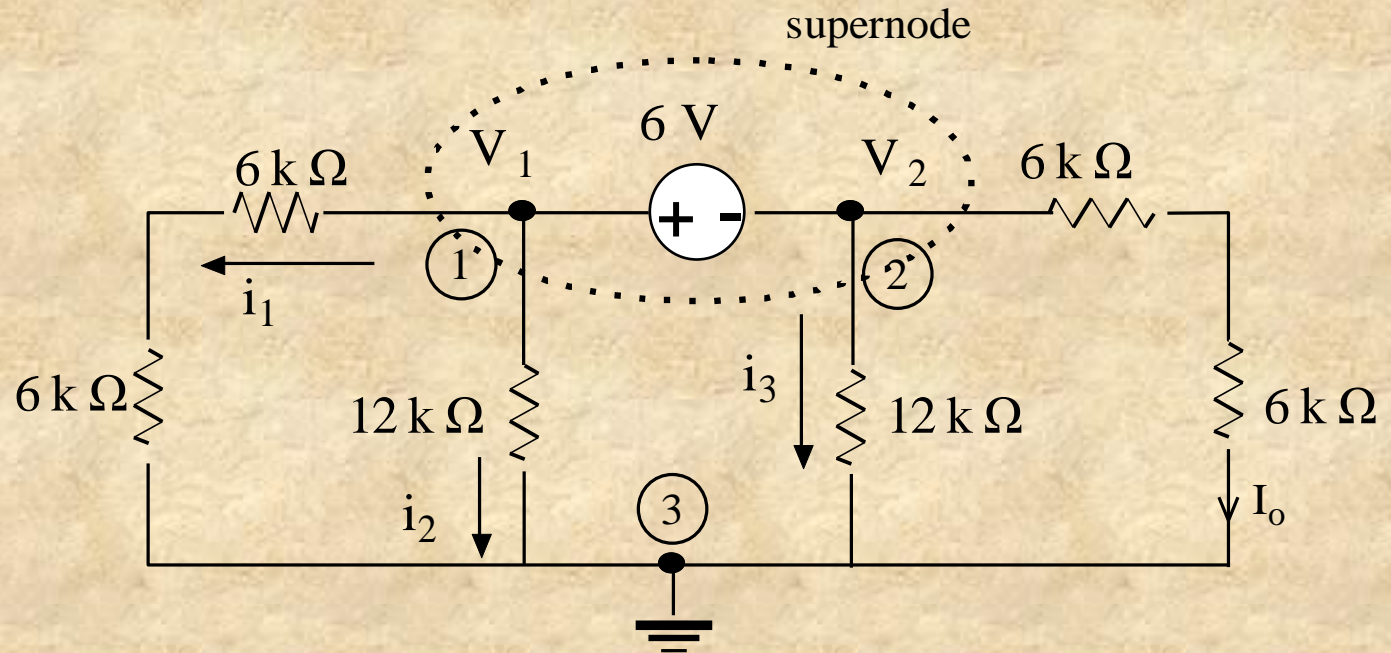This case is called "**super node**" case.



Find I_0

- # of essential nodes = $N = 3$
- “Super node: is the voltage source and the two connecting nodes
- # of equations = $N - 1 - 1 = 3 - 1 - 1 = 1$

Reference node Super node

But we need (2) equations to find the two unknowns V_1 and V_2

⇒ There is an equation that describe the super node.

Apply KCL at the super node :

$$i_1 + i_2 + i_3 + I_0 = 0$$

$$\frac{V_1}{12k} + \frac{V_1}{12k} + \frac{V_2}{12k} + \frac{V_2}{12k} = 0$$

$$\frac{V_1}{6k} + \frac{V_2}{6k} = 0 \quad \dots\dots(1)$$

The super node is described by:

$$V_2 + 6 = V_1 \quad \dots\dots(2)$$

$$\begin{bmatrix} \frac{1}{6k} & \frac{1}{6k} \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 6 \end{bmatrix}$$


$$V_1 = 3 \text{ V}$$

$$V_2 = -3 \text{ V}$$

$$\Rightarrow I_0 = \frac{V_2}{12k} = \frac{-3}{12k} = -0.25 \text{ mA}$$

Example:

Circuits with dependent voltage sources

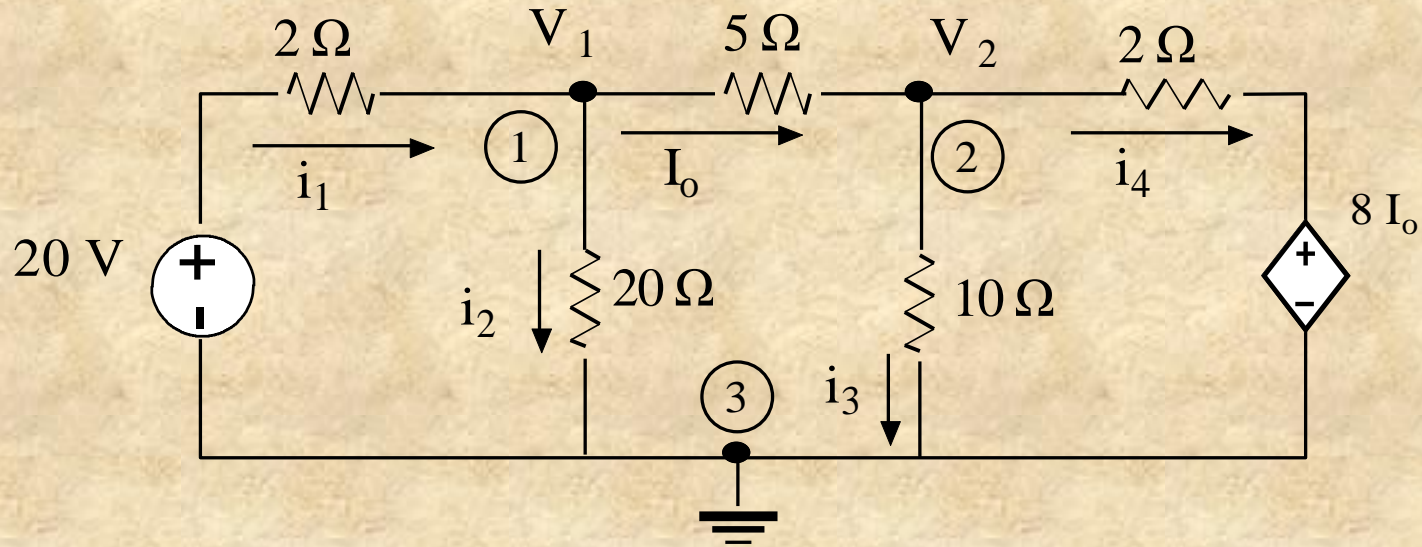

Find I_0 ?

$N = 3$



$N-1 = 2$ equations

KCL at node (1):

$$i_1 = i_2 + I_0$$

$$\frac{20 - V_1}{2} = \frac{V_1}{20} + \frac{V_1 - V_2}{5}$$

$$10 - \frac{V_1}{2} = \frac{V_1}{20} + \frac{V_1 - V_2}{5}$$

$$\left(\frac{1}{2} + \frac{1}{20} + \frac{1}{5} \right) V_1 - \frac{1}{5} V_2 = 10$$

$$\frac{3}{4} V_1 - \frac{1}{5} V_2 = 10 \quad \dots\dots(1)$$

$$I_0 = i_3 + i_4$$

$$\frac{V_1 - V_2}{5} = \frac{V_2}{10} + \frac{V_2 - 8I_0}{2}$$

$$\frac{V_1 - V_2}{5} - \frac{V_2}{5} = \frac{V_2}{10} + \frac{V_2}{2} - 4\left(\frac{V_1 - V_2}{5}\right)$$

$$5\left(\frac{V_1 - V_2}{5}\right) = \frac{V_2}{10} + \frac{V_2}{2}$$

$$V_1 - V_2 = \frac{V_2}{10} + \frac{V_2}{2}$$

$$V_1 - \left(1 + \frac{1}{10} + \frac{1}{2}\right)V_2 = 0$$

$$V_1 - \frac{8}{5}V_2 = 0 \quad \dots\dots(2)$$

$$\begin{bmatrix} 3 & -1 \\ 4 & 5 \\ 1 & -8 \\ & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$V_1 = 16 \text{ V}$$

$$V_2 = 10 \text{ V}$$

$$I_0 = \frac{V_1 - V_2}{5} = \frac{6}{5} = 1.2 \text{ A}$$

Loop Analysis (Mesh)

Mesh analysis : It is a technique in which KVL is used to determine the current in all meshes


of equations needed = # of meshes = $b_e - (n_e - 1)$

Where :

b_e : # of essential branches

n_e : # of essential nodes

Example :

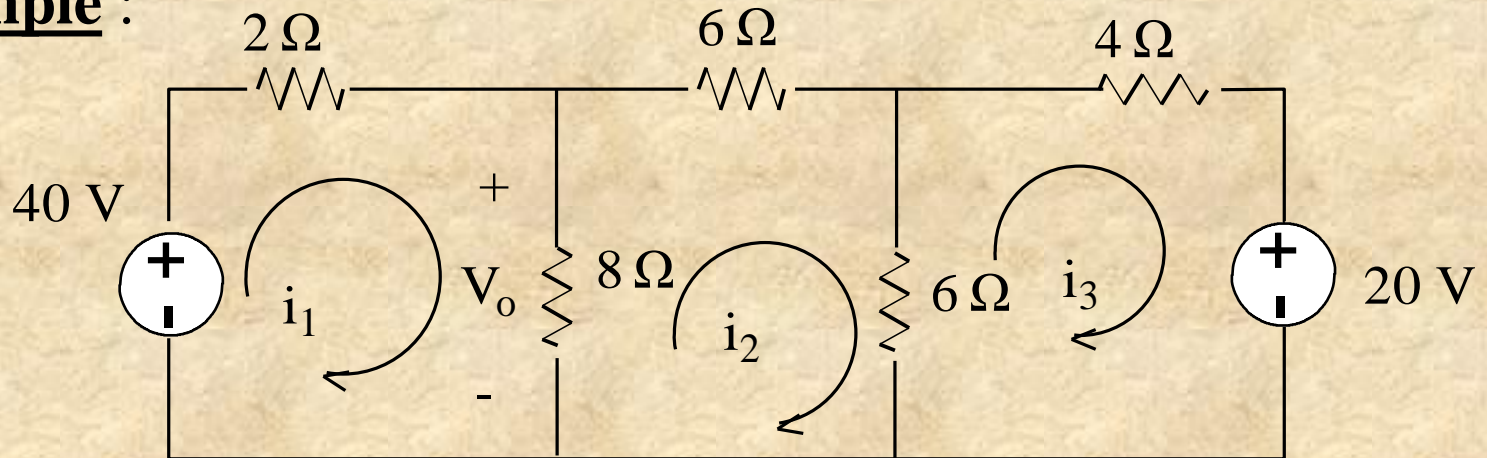

Find V_0 ?

We have (3) meshes

KVL left loop :

$$-40 + 2i_1 + 8(i_1 - i_2) = 0$$
$$10i_1 - 8i_2 + 0i_3 = 40 \quad \dots\dots(1)$$

KVL middle loop: $8(i_2 - i_1) + 6i_2 + 6(i_2 - i_3) = 0$
 $-8i_1 + 20i_2 - 6i_3 = 0$

KVL right loop : $20 + 6(i_3 - i_2) + 4i_3 = 0$
 $0i_1 - 6i_2 + 10i_3 = -20$

$$\begin{bmatrix} 10 & -8 & 0 \\ -8 & 20 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \\ -20 \end{bmatrix}$$


$$i_1 = 5.6 \text{ A} \quad , i_2 = 2 \text{ A} \quad , i_3 = -0.8 \text{ A}$$

$$V_0 = 8(i_1 - i_2) = 8(5.6 - 2) = 8(3.6)$$

$$V_0 = 28.8 \text{ V}$$

Example:

Mesh with dependent source

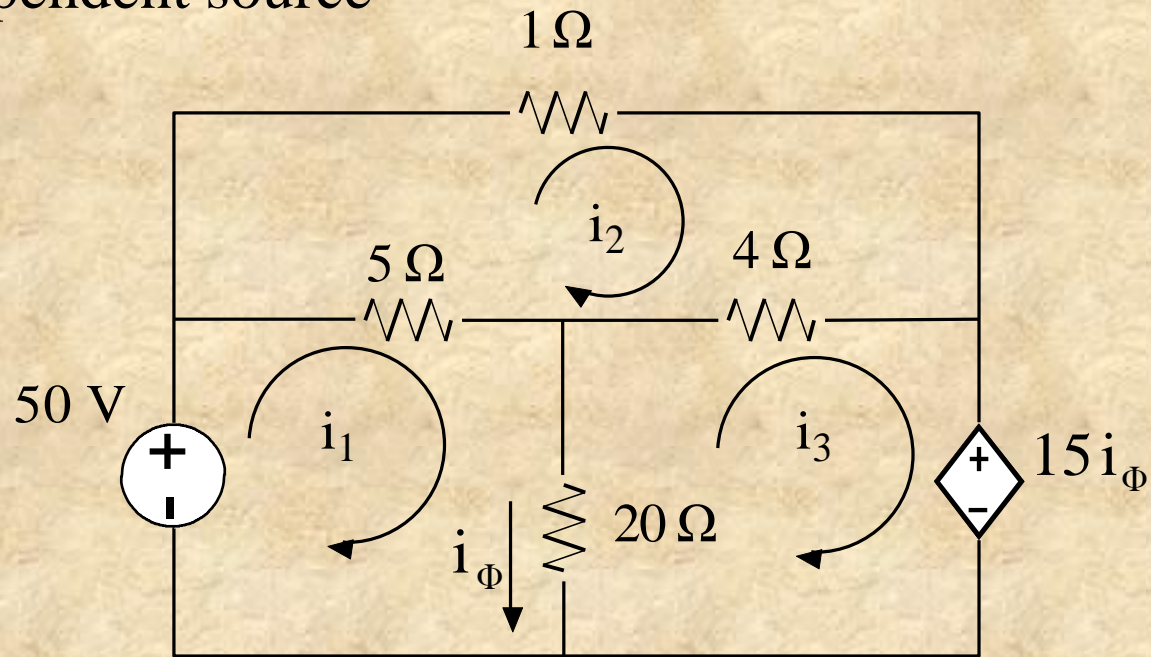

of meshes = 3 so 3 equations are needed

KVL around mesh 1:

$$-50 + 5(i_1 - i_2) + 20(i_1 - i_3)$$
$$25i_1 - 5i_2 - 20i_3 = 50 \quad \dots\dots(1)$$

$$\begin{aligned} \text{KVL around mesh 2: } & 1i_2 + 4(i_2 - i_3) + 5(i_2 - i_1) = 0 \\ & -5i_1 + 10i_2 - 4i_3 = 0 \quad \dots\dots(2) \end{aligned}$$

$$\begin{aligned} \text{KVL around mesh 3: } & 15i_\phi + 20(i_3 - i_1) + 4(i_3 - i_2) = 0 \\ \text{where } & i_\phi = i_1 - i_3 \end{aligned}$$

$$\therefore 15(i_1 - i_3) + 20(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$-5(i_1 - i_3) + 4(i_3 - i_2) = 0$$

$$-5i_1 - 4i_2 + 9i_3 = 0$$

$$\begin{bmatrix} 25 & -5 & -20 \\ -5 & 10 & -4 \\ -5 & -4 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix}$$


$$i_1 = 29.6 \text{ A}, \quad i_2 = 26 \text{ A}, \quad i_3 = 28 \text{ A}$$

Special Case :

What happens if a current source is located between two meshes




“Super mesh”

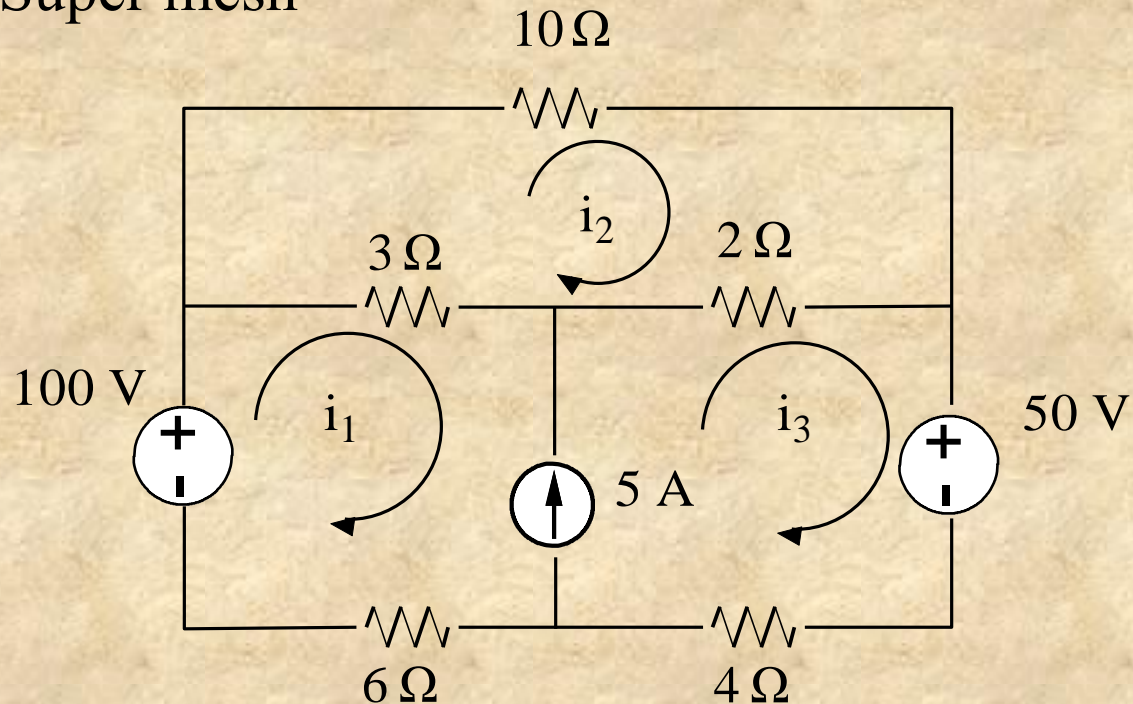

You don't know the voltage across the current source !!



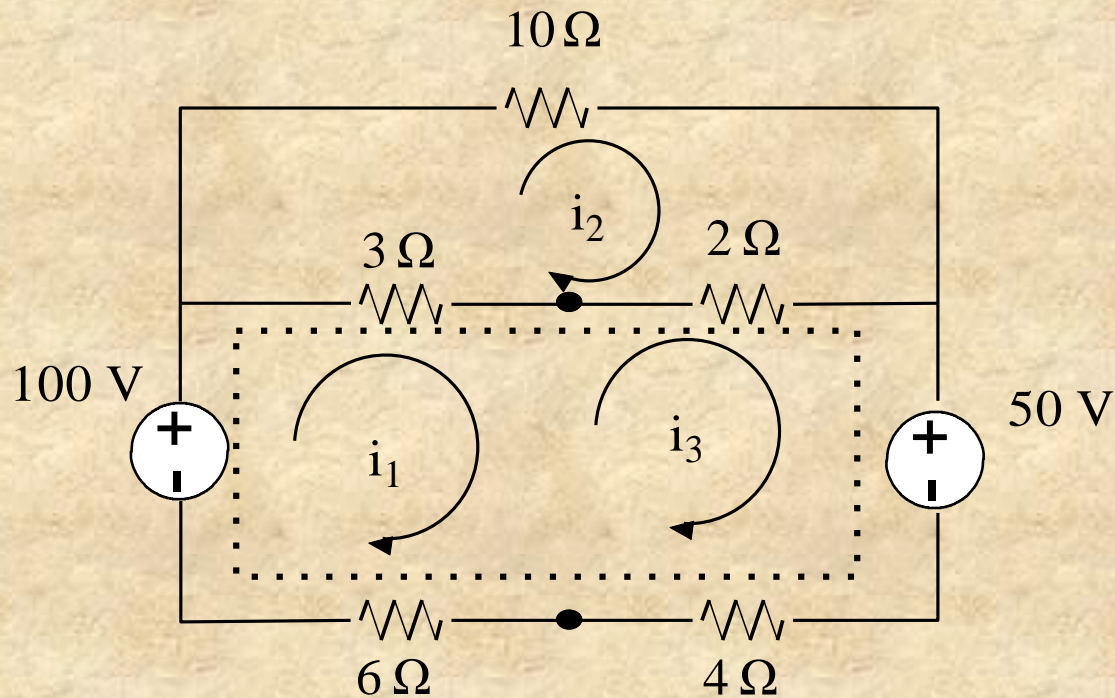Remove the whole branch that includes the current source



Apply KVL around the super mesh

$$-100 + 3(i_1 - i_2) + 2(i_3 - i_2) + 50 + 4i_3 + 6i_1 = 0$$

$$9i_1 - 5i_2 + 6i_3 = 50 \quad \dots\dots(1)$$

KVL around the upper loop:

$$10i_2 + 2(i_2 - i_3) + 3(i_2 - i_1) = 0$$
$$-3i_1 + 15i_2 - 2i_3 = 0 \quad \dots\dots(2)$$

We also know


$$i_3 - i_1 = 5 \text{ A}$$
$$-i_1 + 0i_2 + i_3 = 5 \quad \dots\dots(3)$$

$$i_1 = 1.75 \text{ A}$$

$$i_2 = 1.25 \text{ A}$$


$$i_3 = 6.75 \text{ A}$$

Example:

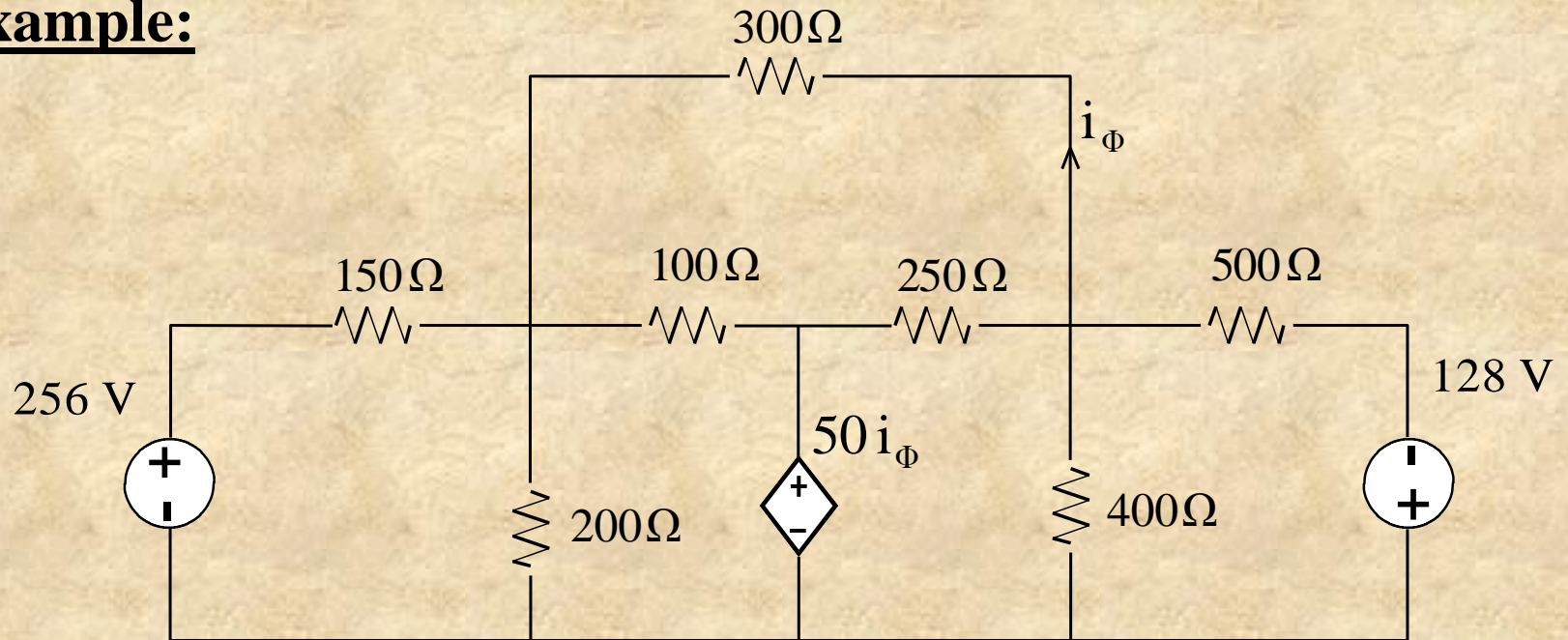

Use nodal analysis and loop analysis to find power in the 300 (Ω) resistor ?

Nodal Analysis :

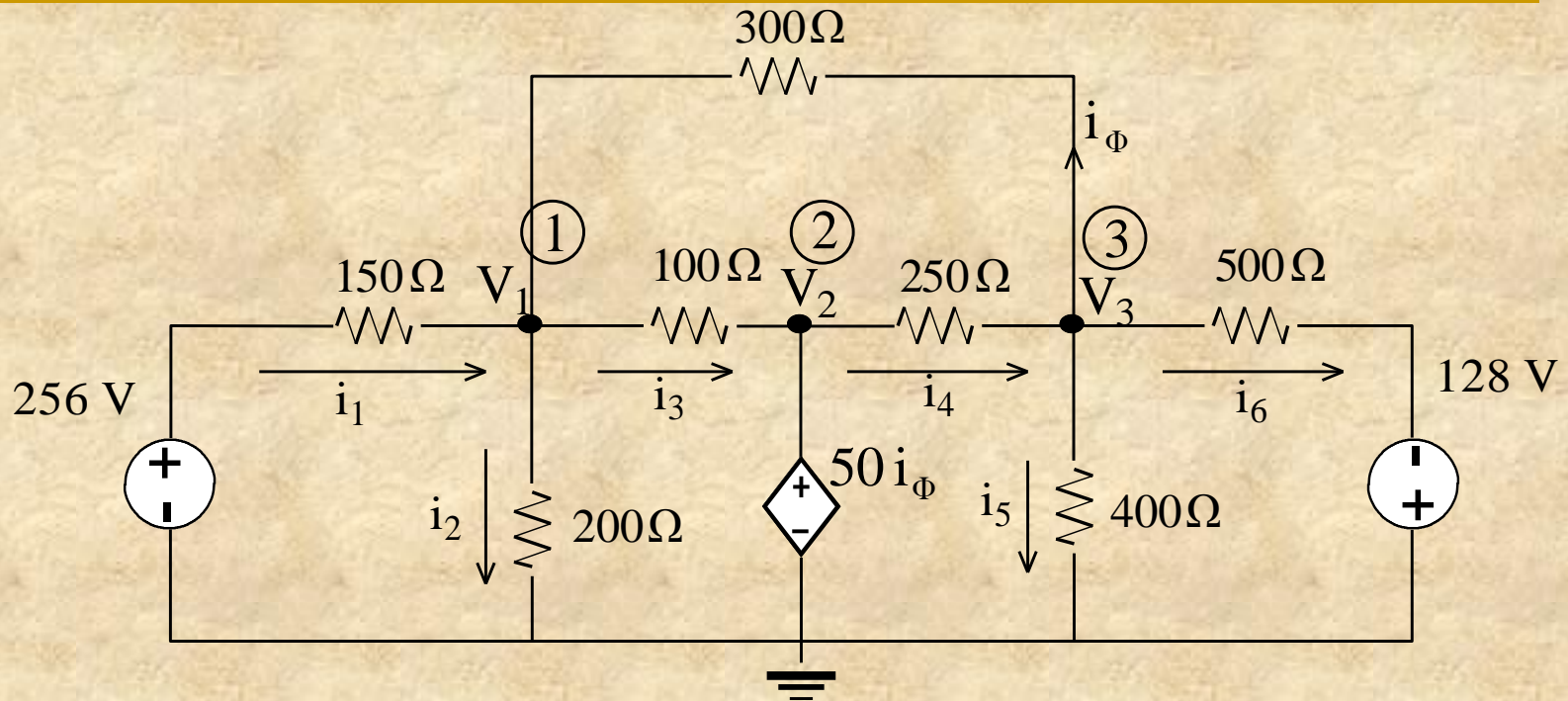

KCL at node (1): $i_1 + i_\phi - i_2 - i_3 = 0$

$$\frac{256 - V_1}{150} + \frac{V_3 - V_1}{300} - \frac{V_1}{200} - \frac{V_1 - V_2}{100} = 0$$

$$V_1 \left(\frac{1}{150} + \frac{1}{300} + \frac{1}{200} + \frac{1}{100} \right) - \left(\frac{1}{100} \right) V_2 - \left(\frac{1}{300} \right) V_3 = \frac{256}{150}$$

$$0.0250 V_1 - 0.01 V_2 - 0.003333 V_3 = 1.7067 \quad \dots\dots(1)$$

KCL at node (3):

$$i_4 - i_5 - i_6 - i_\phi = 0$$

$$\frac{V_2 - V_3}{150} - \frac{V_3}{400} - \frac{V_3 - (-128)}{500} - \frac{V_3 - V_1}{300} = 0$$

$$\frac{V_1}{300} + \frac{V_2}{250} + V_3 \left(\frac{-1}{250} - \frac{1}{400} - \frac{1}{500} - \frac{1}{300} \right) = \frac{128}{500}$$

$$0.0033 V_1 + 0.004 V_2 - 0.0118 V_3 = 0.256 \quad \dots\dots(2)$$

You can notice that

$$V_2 = 50i_\phi$$

$$V_2 = 50 \left(\frac{V_3 - V_1}{300} \right) = \frac{1}{6} V_3 - \frac{1}{6} V_1$$

$$0.166 V_1 + 1 V_2 - 0.1667 V_3 = 0 \quad \dots\dots(3)$$

$$\begin{bmatrix} 0.0383 & -0.01 & -0.0033 \\ 0.0033 & 0.004 & -0.0118 \\ 0.1667 & 1 & -0.1667 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 1.7067 \\ 0.256 \\ 0 \end{bmatrix}$$

$$V_1 = 62.5 \text{ V}$$


$$V_2 = -11.75 \text{ V}$$

$$V_3 = -8 \text{ V}$$

$$i_{\Phi} = \frac{V_2}{50} \Rightarrow i_{\Phi} = -0.235 \text{ A}$$

$$P_{30\Omega} = i_{\Phi}^2 R = (-0.235)^2 (300) = 16.5675 \text{ W}$$

Using loop analysis:

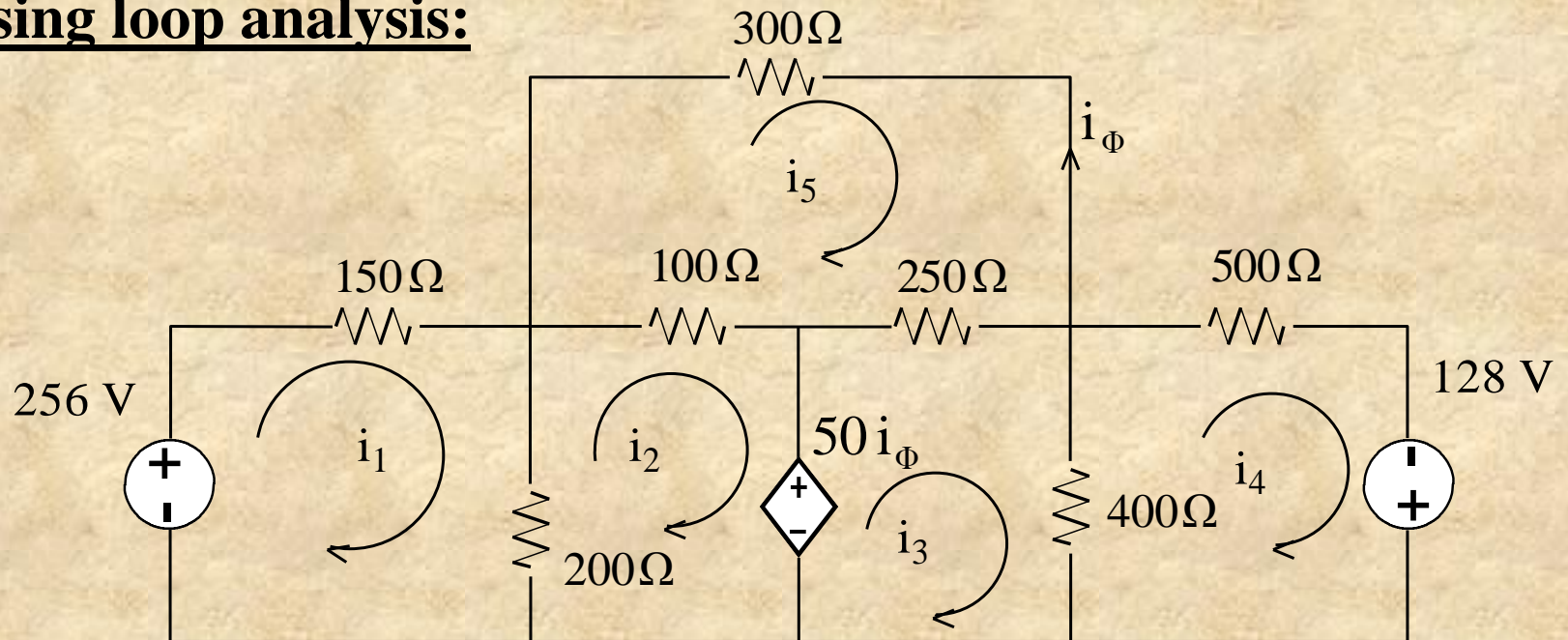

5 meshes



5 equations

KVL around loop (1):

$$150 i_1 + 200 (i_1 - i_2) = 256$$

$$350 i_1 - 200 i_2 = 256 \quad \dots\dots(1)$$

KVL around loop (2):

$$100 (i_2 - i_5) + 50 i_{\Phi} + 200 (i_2 - i_1) = 0$$

$$i_{\Phi} = -i_5$$

$$100 (i_2 - i_5) - 50 i_5 + 200 (i_2 - i_1) = 0$$

$$-200 i_1 + 300 i_2 - 150 i_5 = 0 \quad \dots\dots(2)$$

KVL around loop (3)

$$500 i_4 - 128 + 400 (i_4 - i_3) = 0$$

$$-400 i_3 + 900 i_4 = 128 \quad \dots\dots(4)$$

KVL around loop (4)

$$250 (i_3 - i_5) + 400 (i_3 - i_4) - 50 i_{\Phi} = 0$$

$$650 i_3 - 400 i_4 - 200 i_5 = 0 \quad \dots\dots(3)$$

since $i_{\Phi} = -i_5$

KVL around loop (5)

$$300 i_5 + 250 (i_5 - i_3) + 100 (i_5 - i_2) = 0$$
$$-100 i_2 - 250 i_3 + 650 i_5 = 0 \quad \dots\dots(5)$$

$$\begin{bmatrix} 350 & -200 & 0 & 0 & 0 \\ -200 & 300 & 0 & 0 & -150 \\ 0 & 0 & 650 & -400 & -200 \\ 0 & 0 & -400 & 900 & 0 \\ 0 & -100 & -250 & 0 & 650 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 256 \\ 0 \\ 0 \\ 128 \\ 0 \end{bmatrix}$$

$$i_1 = 1.29 \text{ A}$$

$$i_2 = 0.9775 \text{ A}$$

$$i_3 = 0.22 \text{ A}$$


$$i_4 = 0.24 \text{ A}$$

$$i_5 = 0.235 \text{ A}$$

$$\begin{aligned} P_{300\Omega} &= (i_5)^2 R = (0.235)^2 (300) \\ &= 16.5675 \text{ W} \end{aligned}$$

Example:

Use the loop analysis to find V_{Φ}

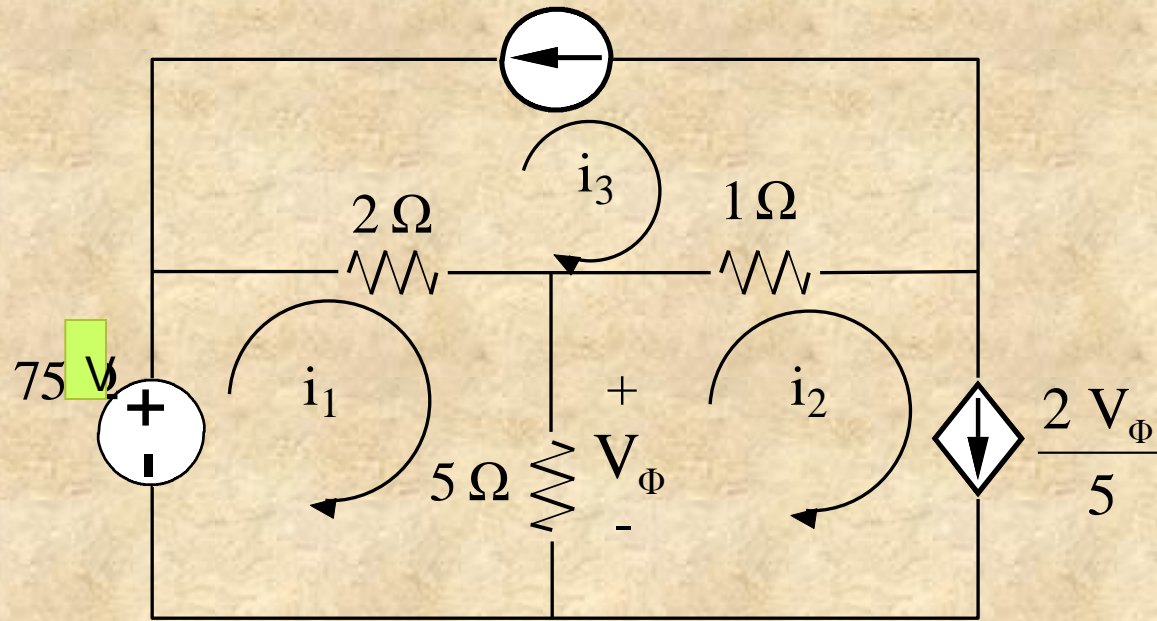

(3) Meshes \Rightarrow (3) equations

$$i_3 = -10A$$

KVL around loop (1):

$$2 (i_1 - i_3) + 5 (i_1 - i_2) - 75 = 0$$

$$7 i_1 - 5 i_2 + 20 - 75 = 0$$

$$7 i_1 - 5 i_2 = 55 \quad \dots\dots(1)$$

Equation of dependent source:

$$i_2 = \frac{2 V_\Phi}{5}$$

$$V_\Phi = 5 (i_1 - i_2)$$

$$i_2 = \left(\frac{2}{5} \right) (5) (i_1 - i_2) = 2 i_1 - 2 i_2$$

$$2 i_1 - 3 i_2 = 0 \quad \dots\dots(2)$$

$$\begin{bmatrix} 7 & -5 \\ 2 & -3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 55 \\ 0 \end{bmatrix}$$

$$i_1 = 15 \text{ A}$$

$$i_2 = 10 \text{ A}$$

$$\begin{aligned} V_{\Phi} &= 5 (i_1 - i_2) \\ &= 5 (15 - 10) = 25 \text{ V} \end{aligned}$$

$$V_{\Phi} = 25 \text{ V}$$